

# ECEN 449 – Microprocessor System Design




## Memories


# Objectives of this Lecture Unit

- Learn about different types of memories
  - SRAM/DRAM/CAM
  - Flash

# SRAM –Static Random Access Memory

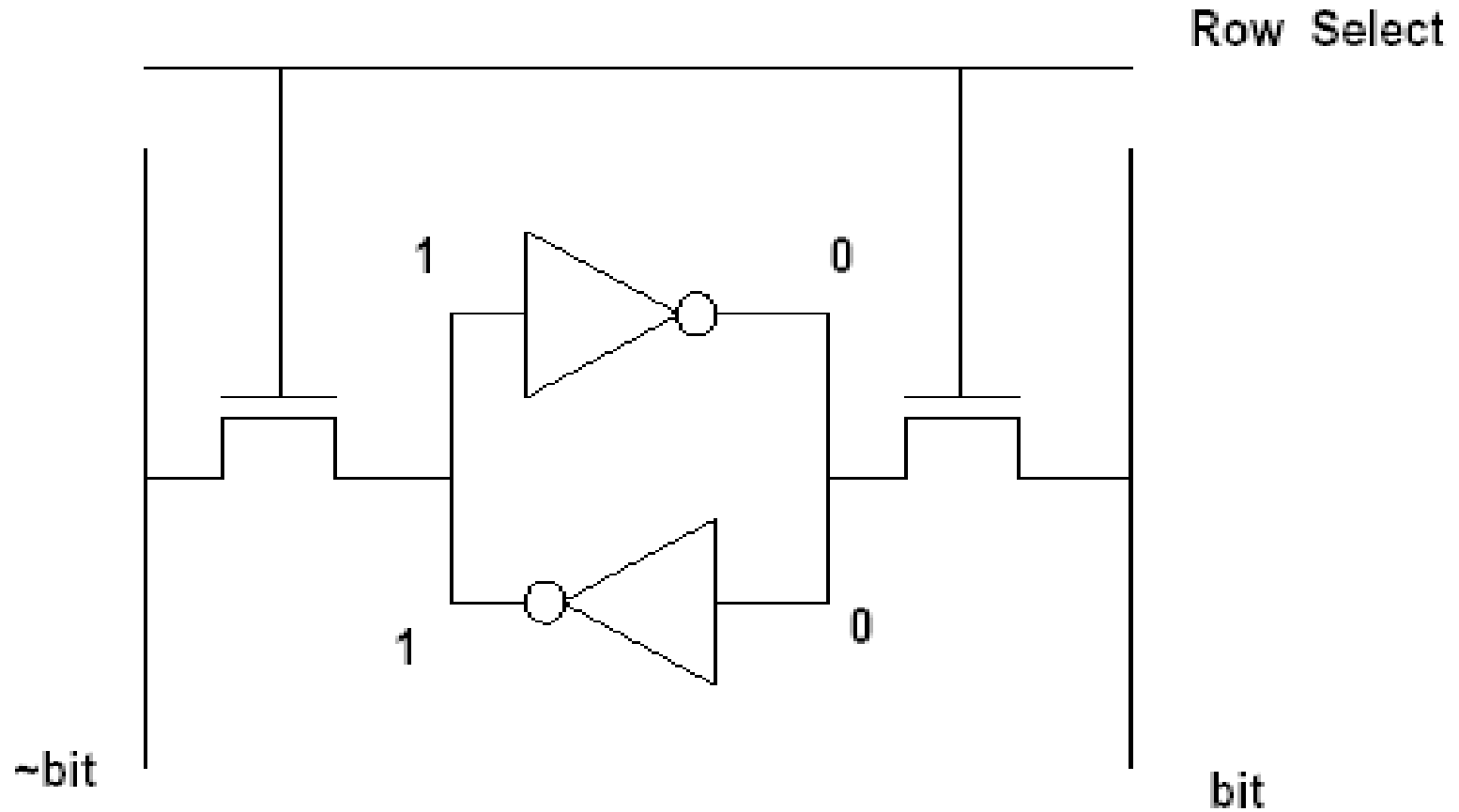

# SRAM – Static Random Access Memory

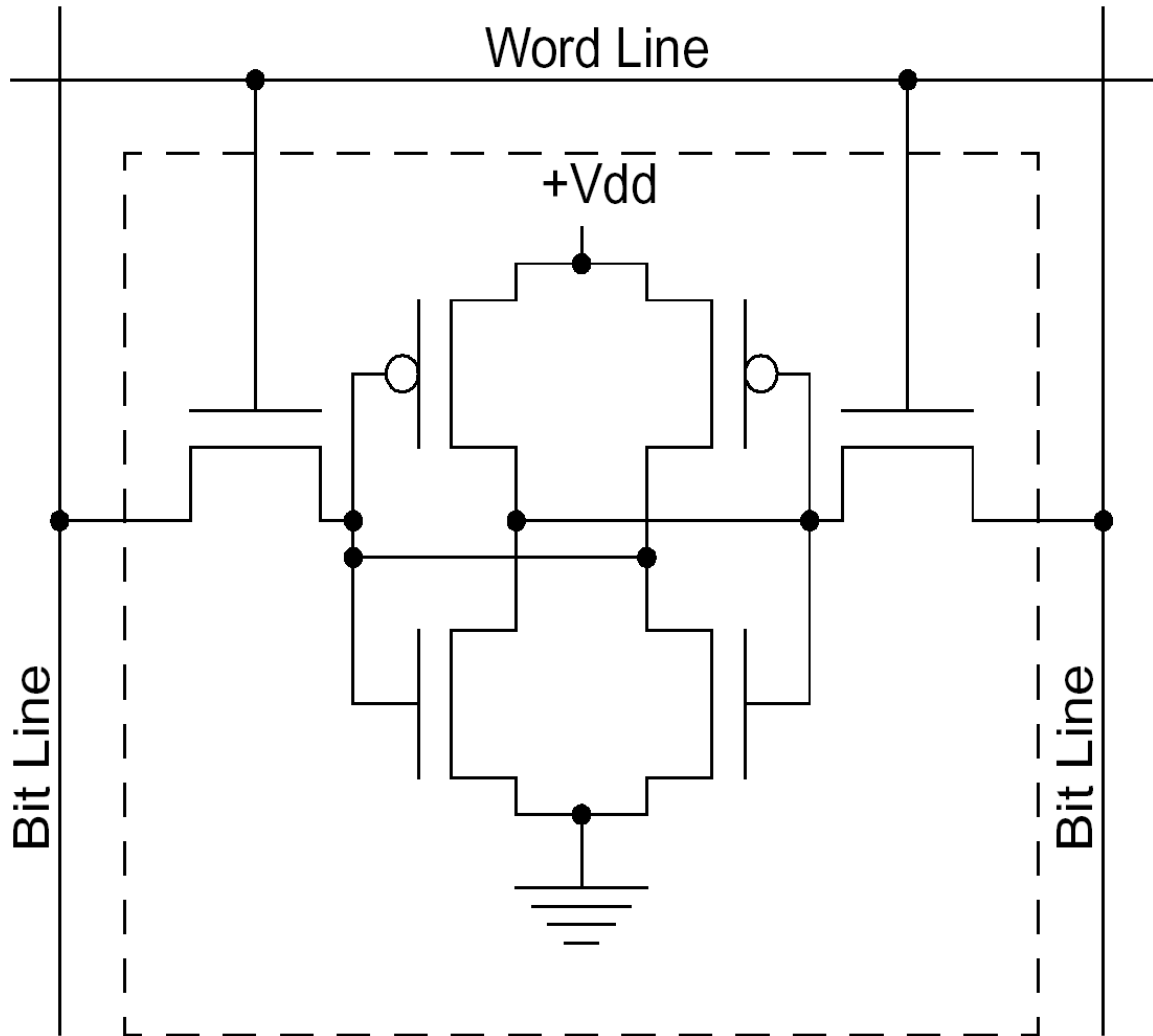


## SRAM function

- When RowSelect = 1, cell can be written or read
- Cell written by precharging bit/bit~ lines to required value
  - Write drivers more powerful than NOT gates
- Cell read by comparing bit/bit~ lines


# Multi-ported SRAM

- Sometimes we want to read and write at the same time
- For example, registers in a processor chip
  - Support 2 reads and 1 write at the same time
- Add more bit and word lines.

# Dual Ported SRAM

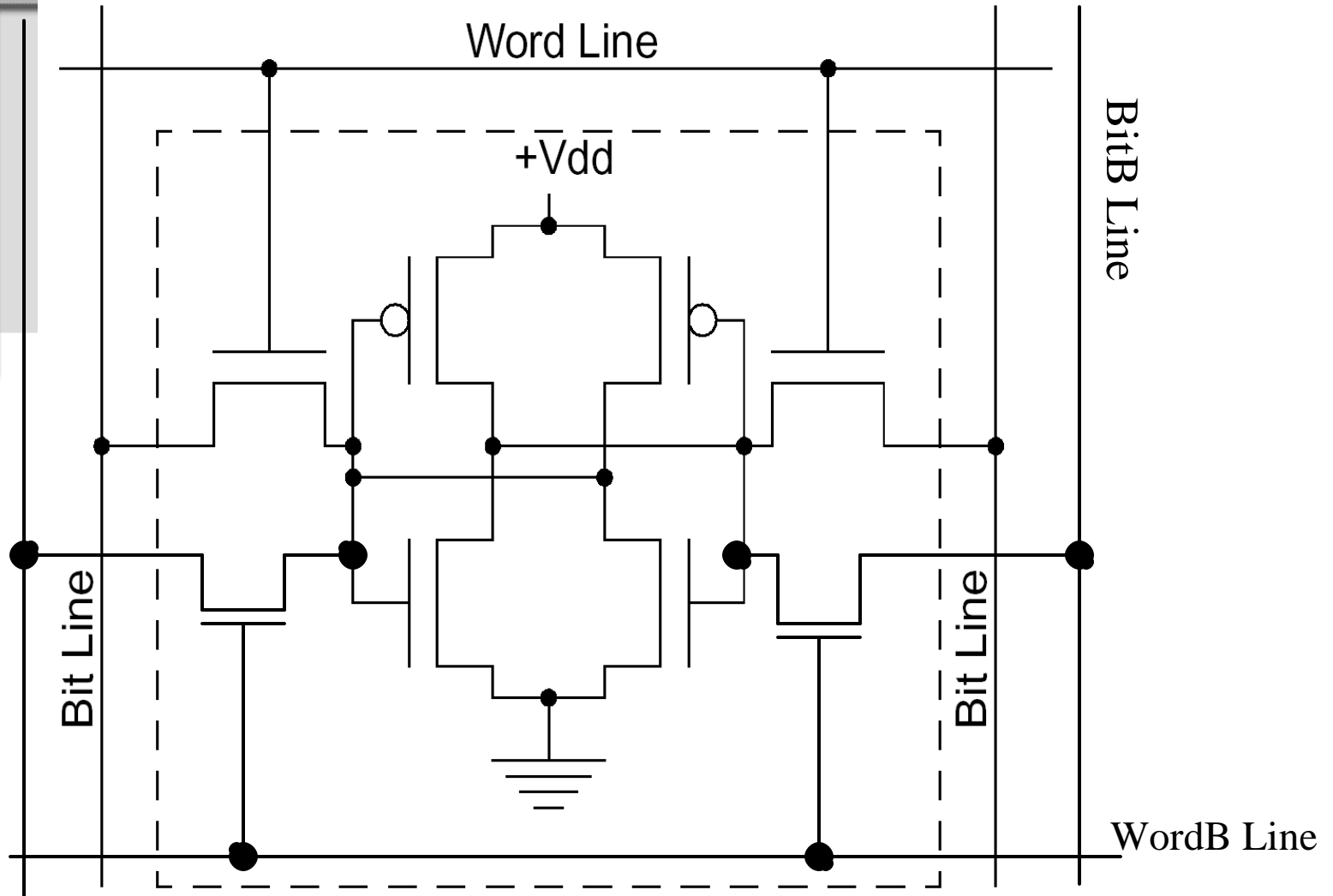


# Dual Ported SRAM – Second Design

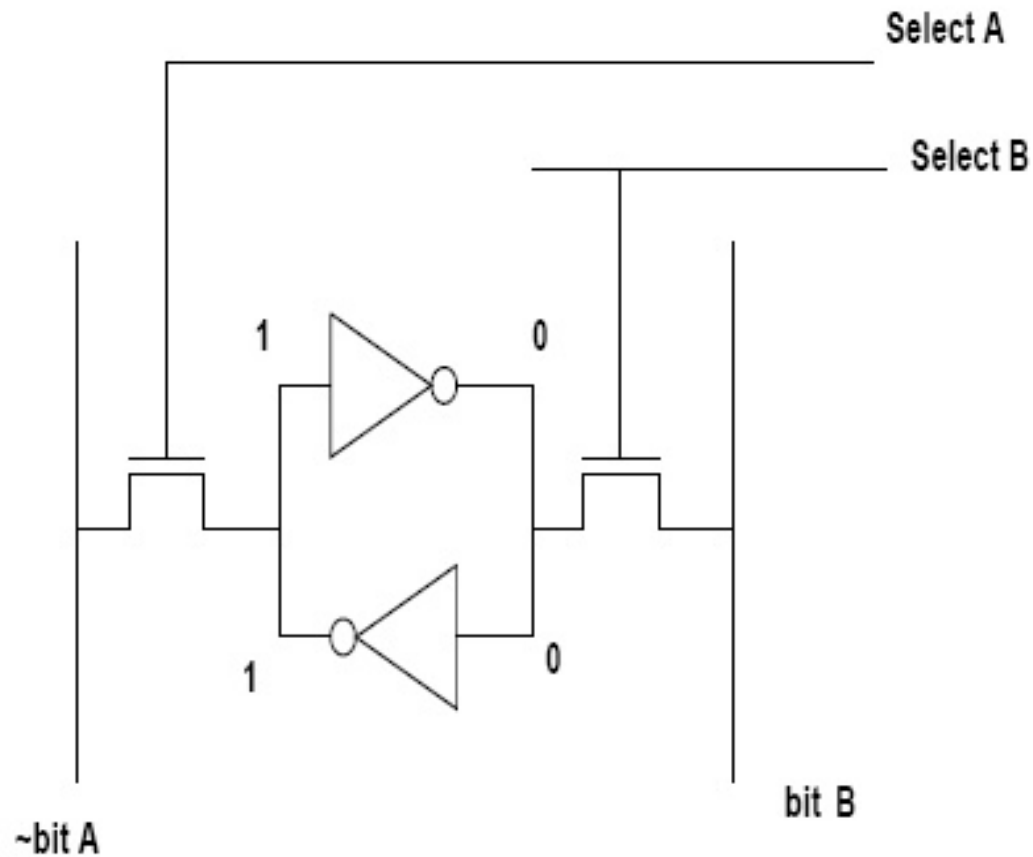





## Register cell – 2 Reads and 1 Write

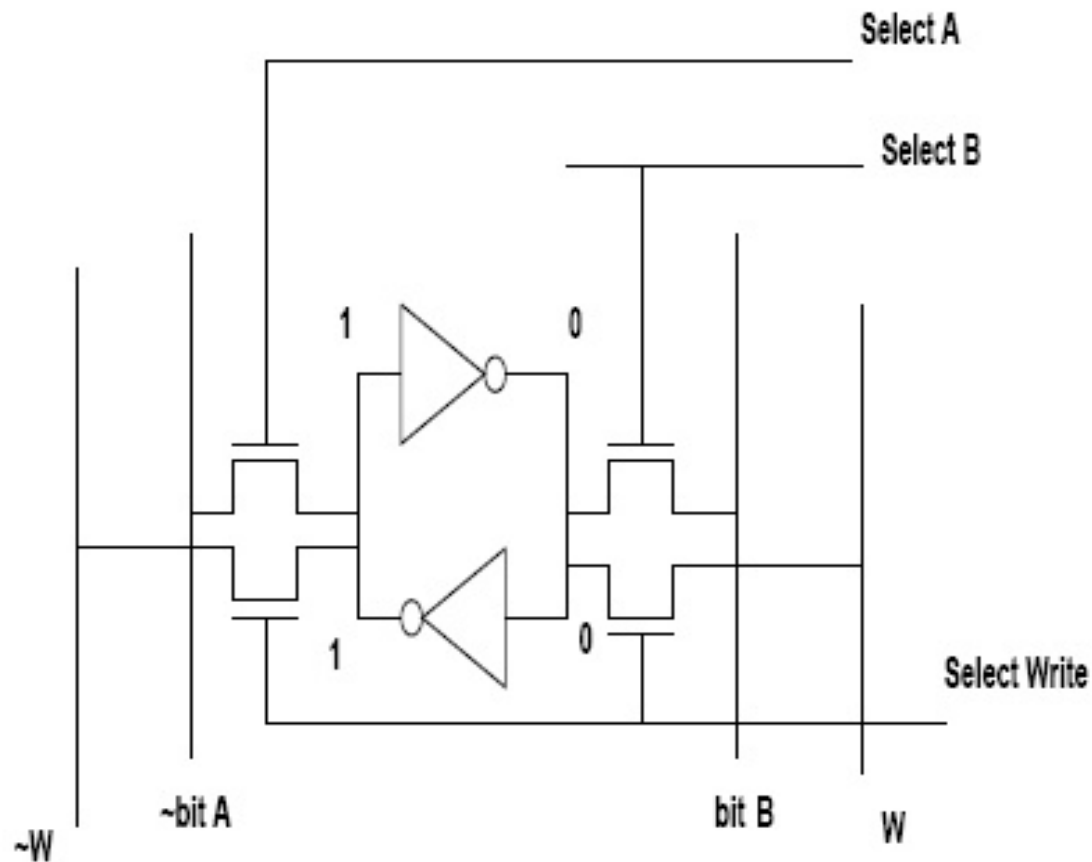


# SRAM 16 words, each word = 4bits

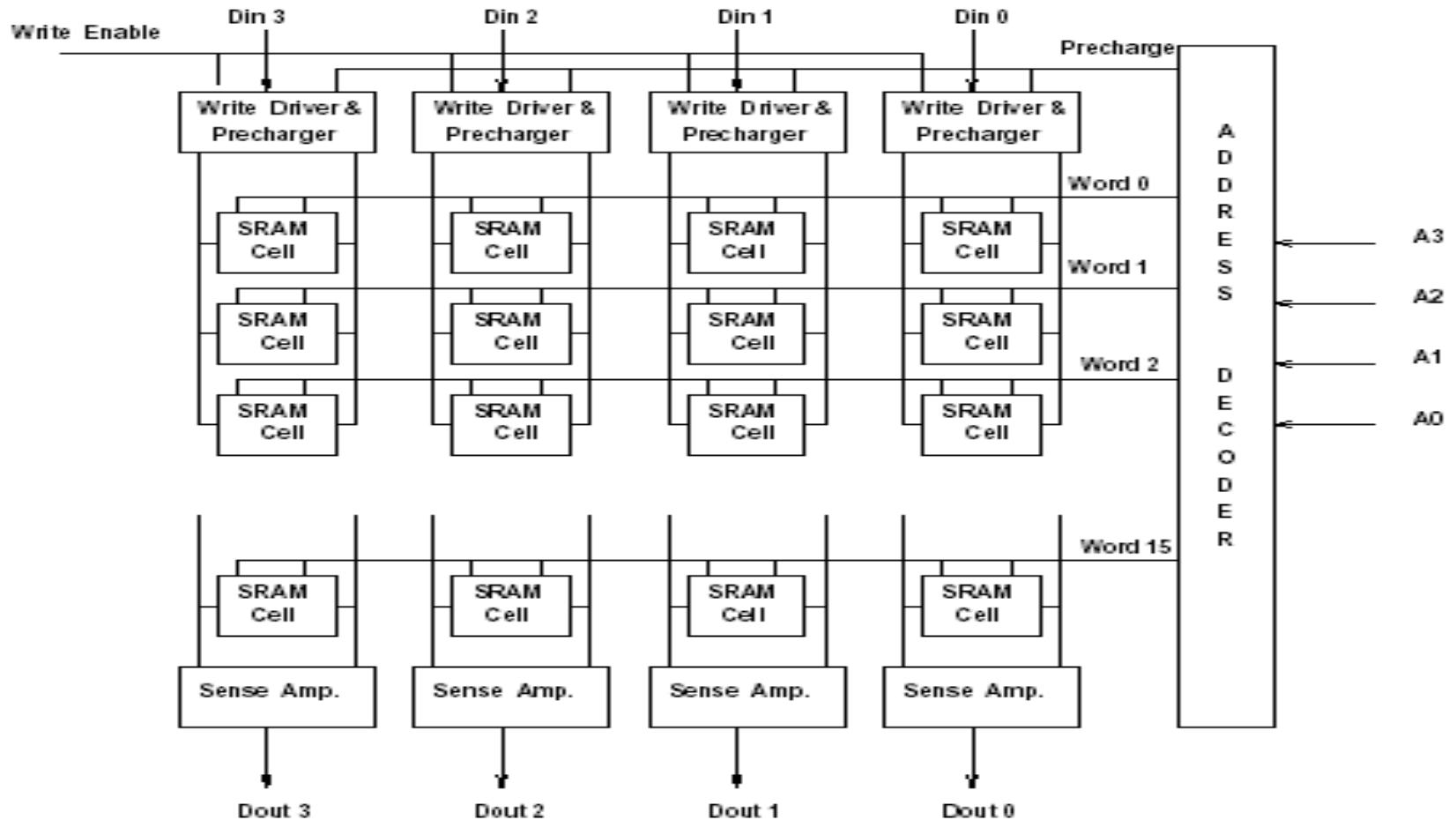

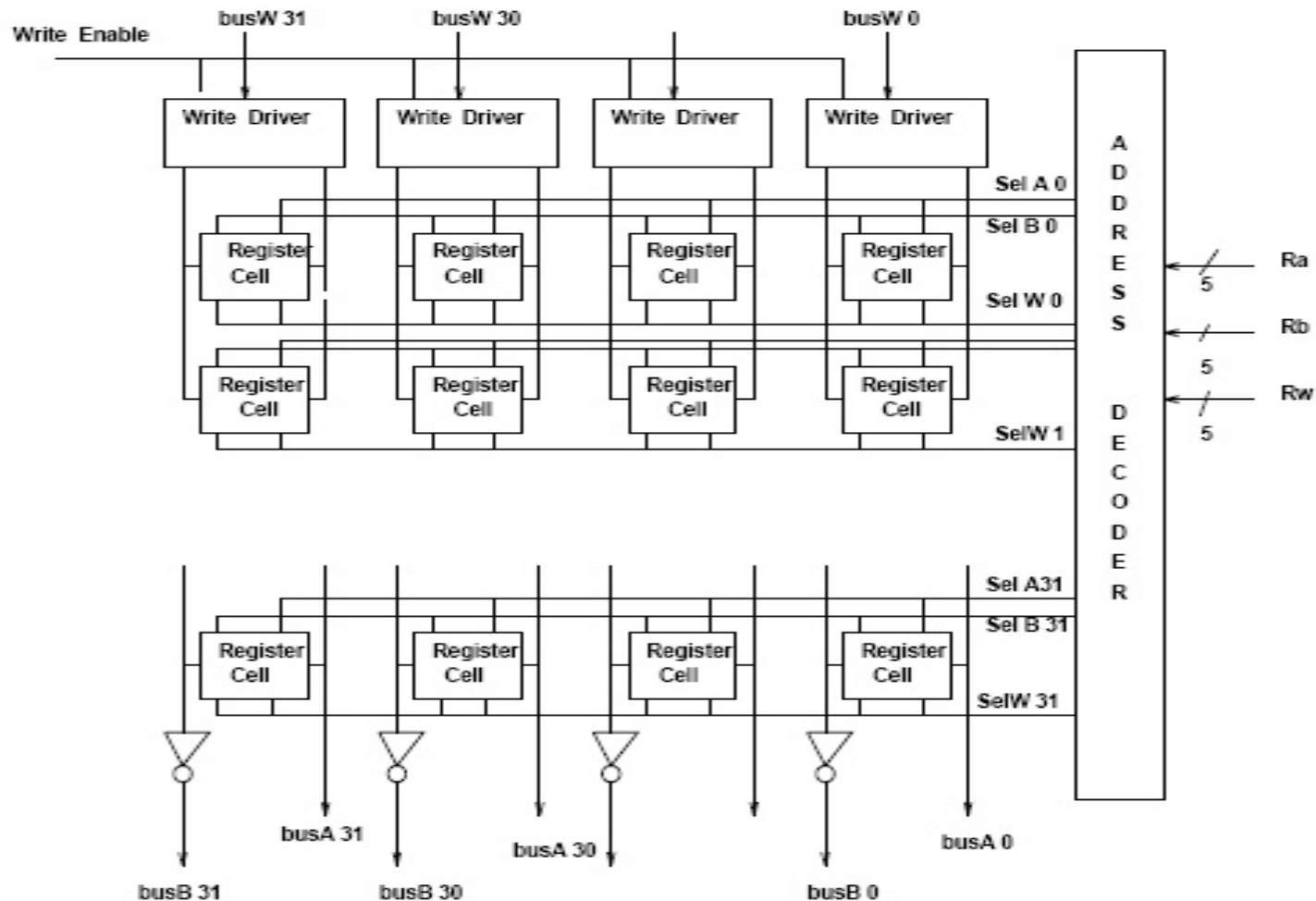
# Register File – 32 Registers –each 32 bits



# SRAM – Access timing cycles

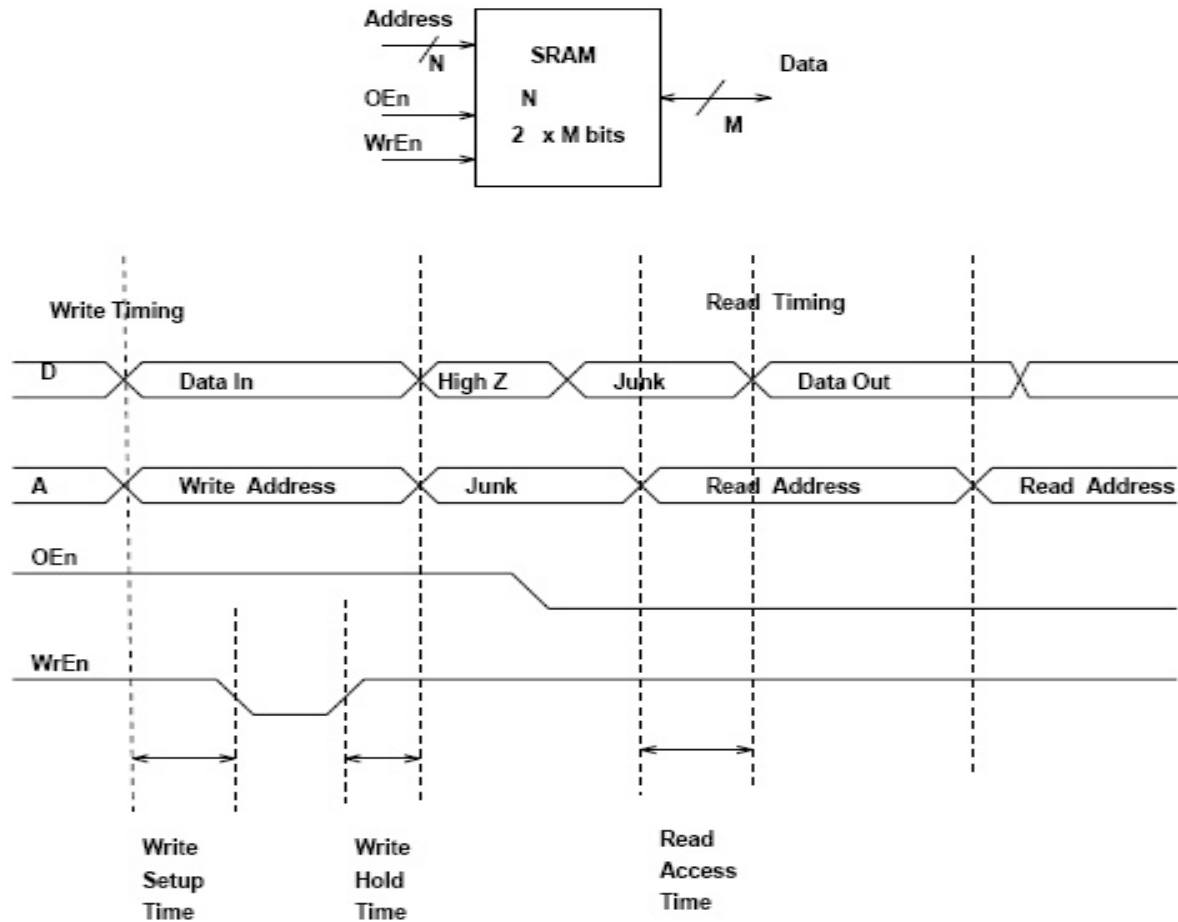


# DRAM – Dynamic RAM

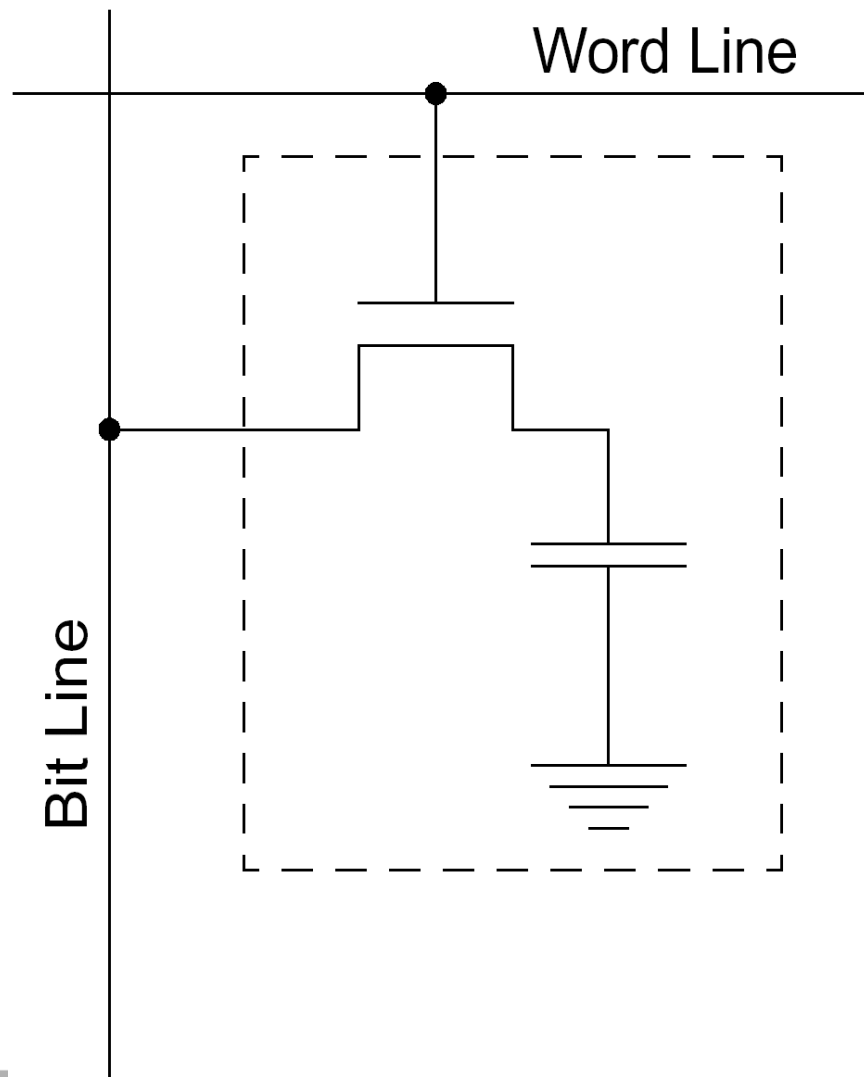


## DRAM function

- Charge on the capacitance remembers 1
- Charge dissipates over time
  - Over time 1 becomes 0
- Need to refresh memory
- To read, Row Select = 1, charge is transferred to bit line
  - Capacitor discharged
  - Every read requires rewriting read value back

# DRAM organization

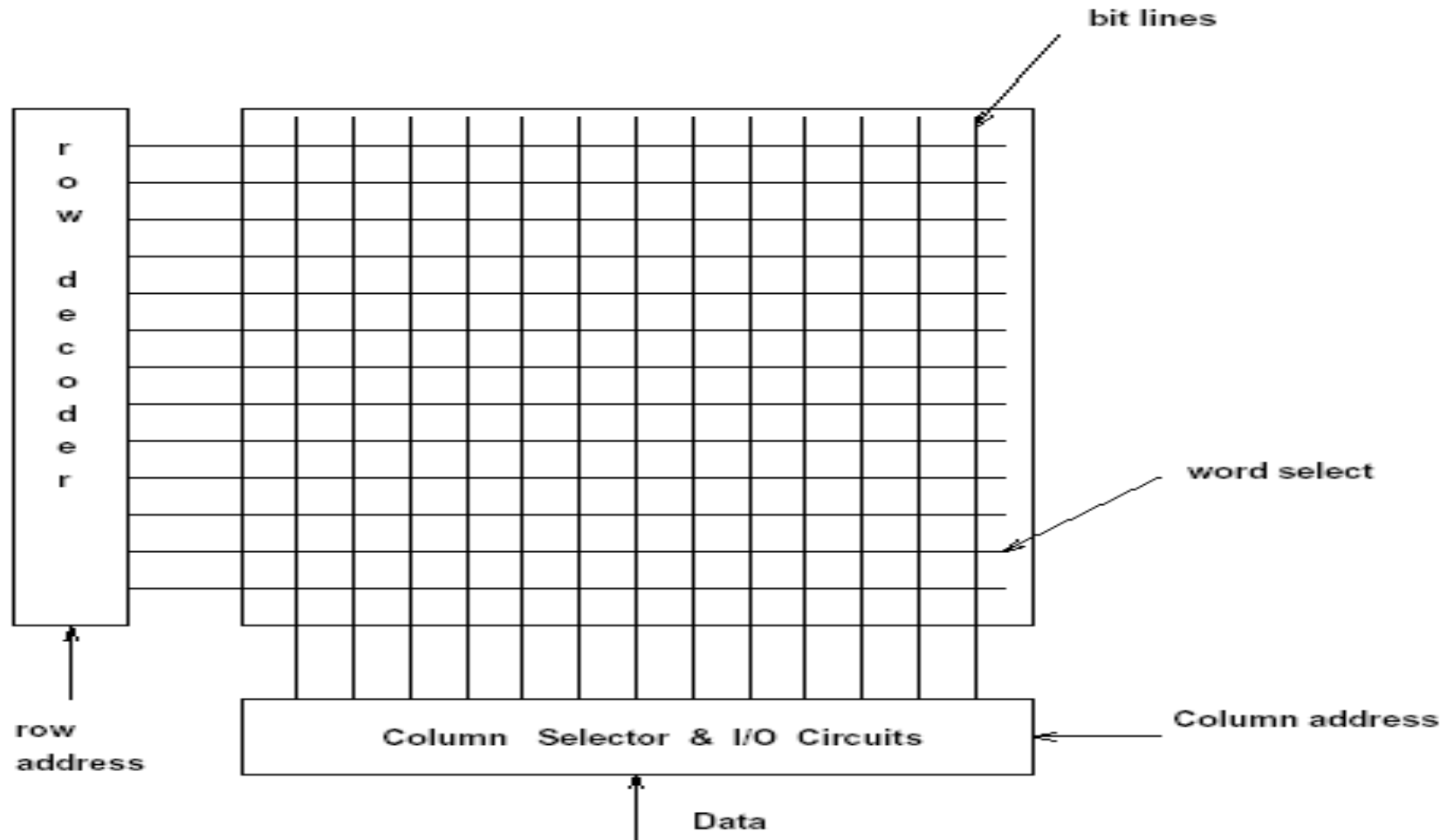

# DRAM organization

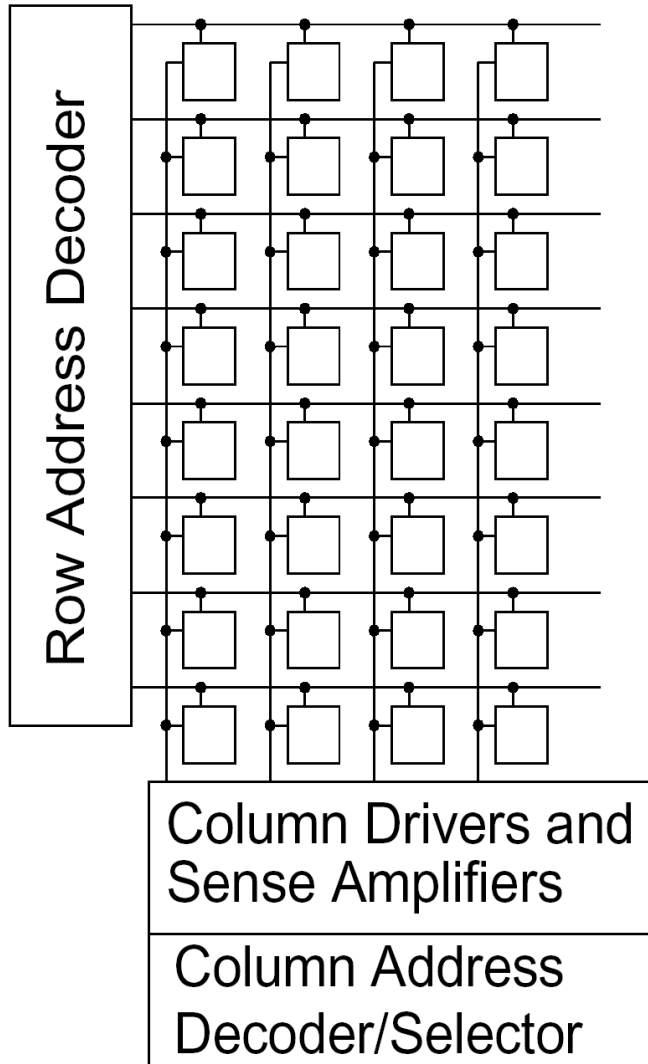


- Must amplify small charge on cell cap many times to drive off-chip
  - Makes it slower than SRAM
- Select which of millions of bits to read or write




# DRAM organization

- Typically Din, Dout combined into D pins
- WrEn (WriteEnable) and OEn (Output Enable) distinguish whether Data pins are input or output
  - WrEn asserted, OEn deasserted D = Din (Write Cycle)
  - WrEn deasserted, OEn asserted D = Dout (Read cycle)
- Column and Row addresses are serially input on address pins
  - Column Address Select (CAS), Row Address Select (RAS) lines used
  - RAS asserted => latch address as row address
  - CAS asserted => latch address as column address

# DRAM Read Timing

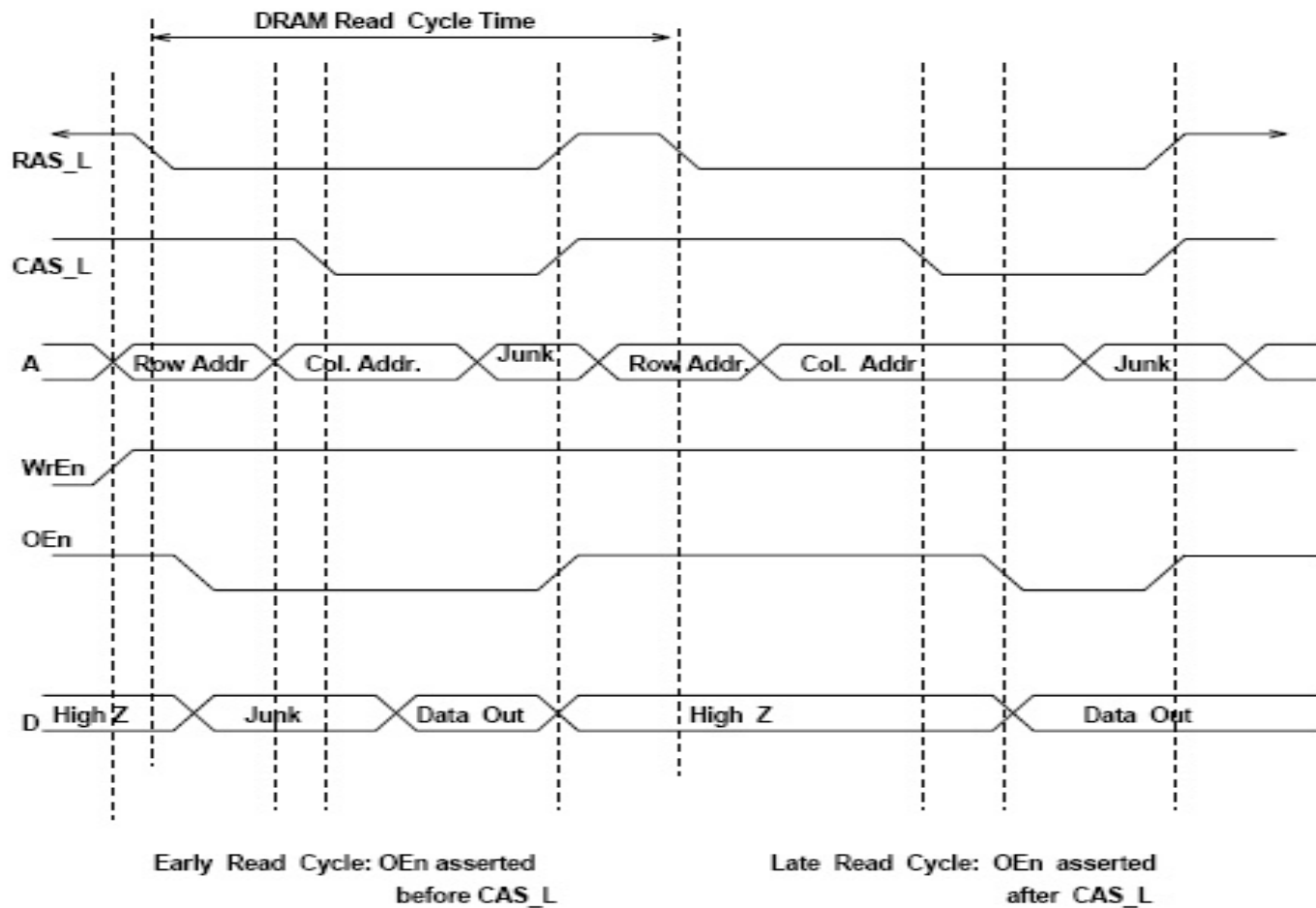

# DRAM Write Timing

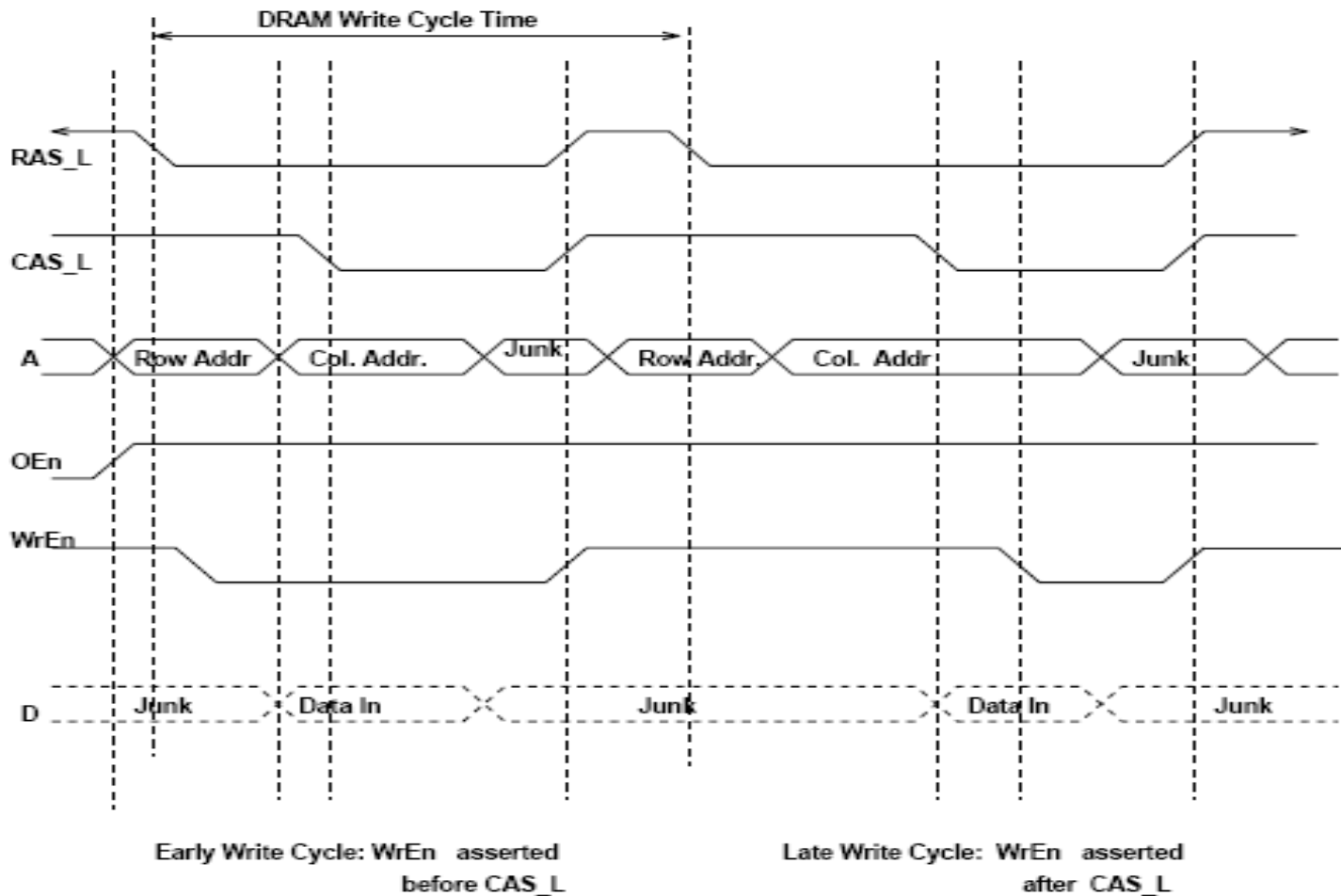

# SRAM/DRAM comparison

- Speed
  - SRAM +, DRAM –
  - Use SRAM for cache, network buffers, etc.
- Volatility
  - SRAM retains data while power is on
  - DRAM must be refreshed every few milliseconds
- Cost
  - SRAM -, DRAM ++
  - Use DRAM for big, cheap memories
- Overhead
  - SRAM +, DRAM – (due to refreshing and clocks)
  - Use SRAM for small memories, DRAM for big

# Content Addressable Memory (CAM)

- In normal memories, we access data stored at a particular address
  - We give the address as input, to write/read data
- What if we want to access data by its contents?
  - Content addressable memories
- Used extensively in network routers/switches
- Look up CAM tutorial at <http://www.pagiamtzis.com/pubs/pagiamtzis-jssc2006.pdf>


## Example use of CAMs –Network Router

<b>Destination Address</b>	<b>Next Hop –Output Port</b>
0011 1xxx	1
0010 0000	2
0010 0100	3
Xxxx xxxx	1

## Example use of CAMs –network routers


- Given a destination address, we want to find which way to send the packet
- The routing table as organized as shown
- We want to match the contents of the routing table entries to the destination address to find the direction in which to send the packet
- Addresses may be completely or partially specified
  - Don't cares or a concise way of representing many addresses
  - Saves space in the routing table

# Binary CAMs

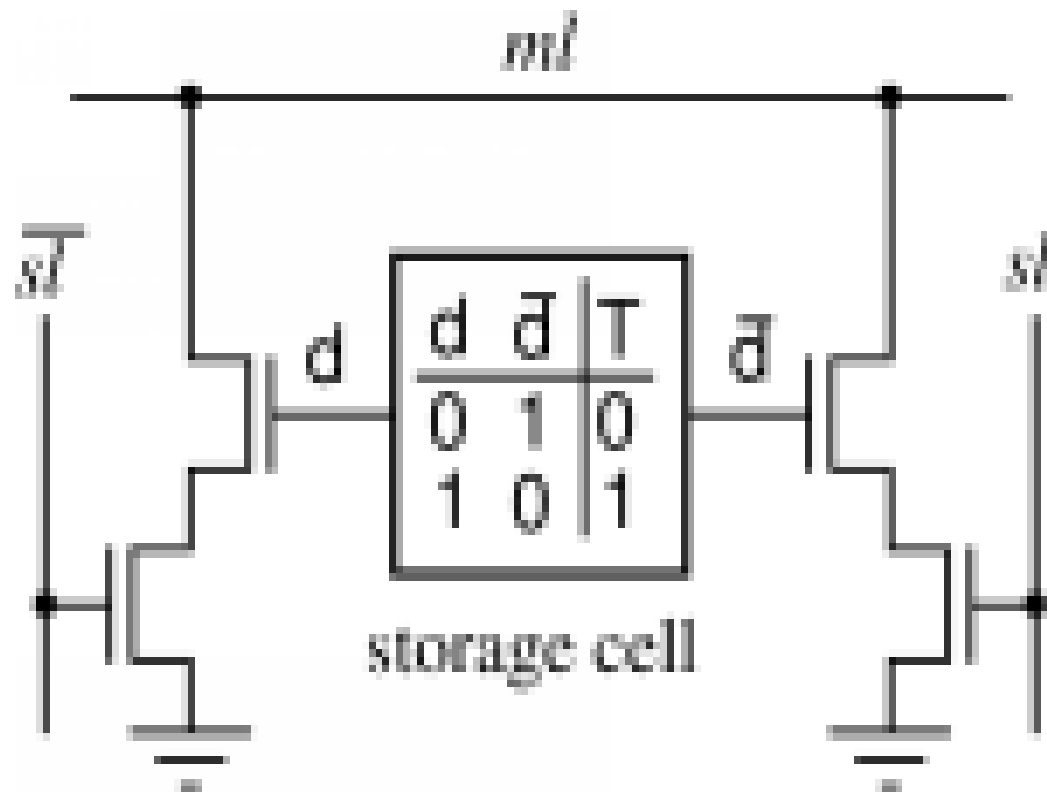




# CAM Cell

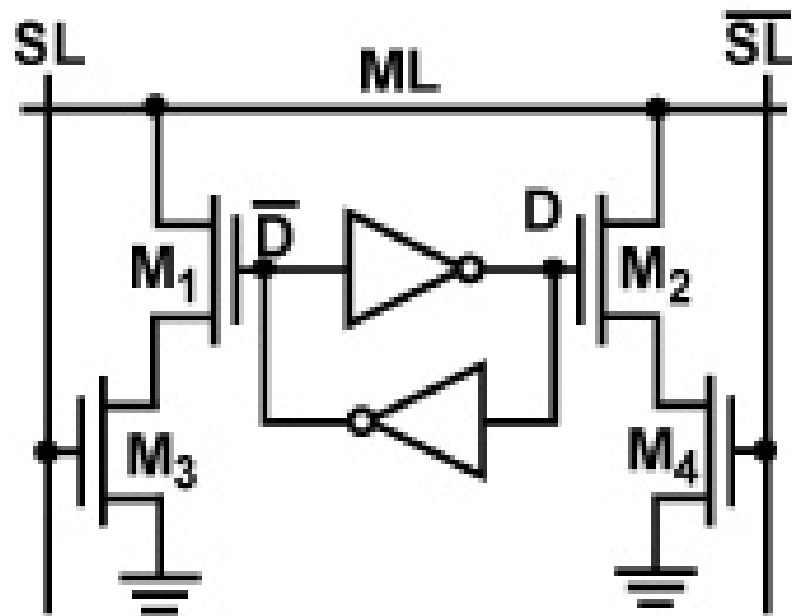

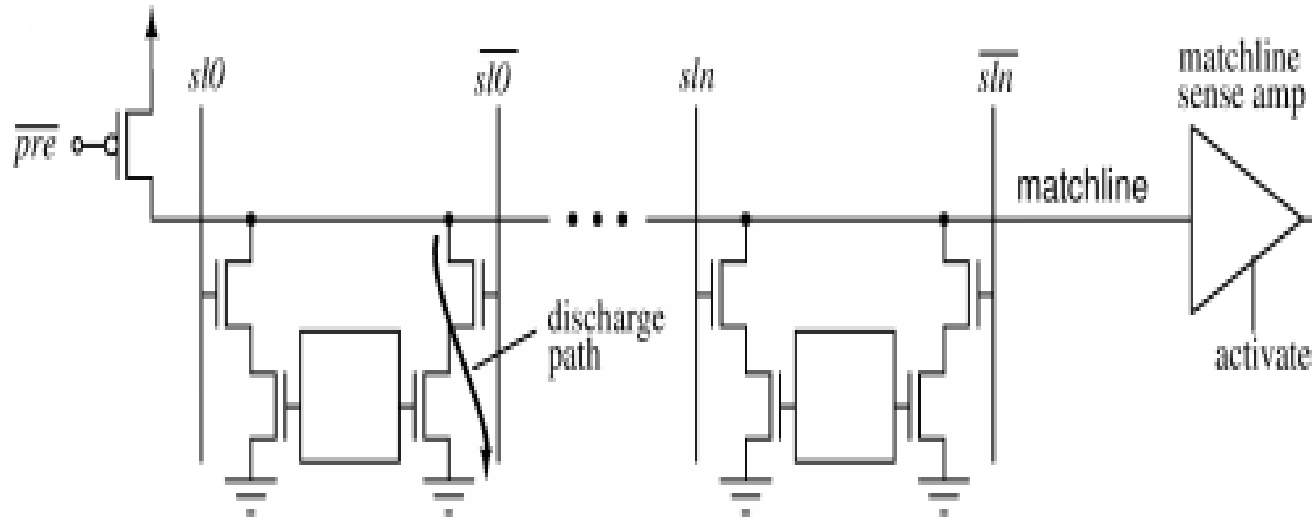
# Binary CAMs

- CAM can be designed as 10-Transistor cell
  - Storage cell = 6-transistor SRAM
- Match line is precharged high
- When the Content in the cell doesn't match the data on the search lines, match line is discharged => no match




# CAM architecture

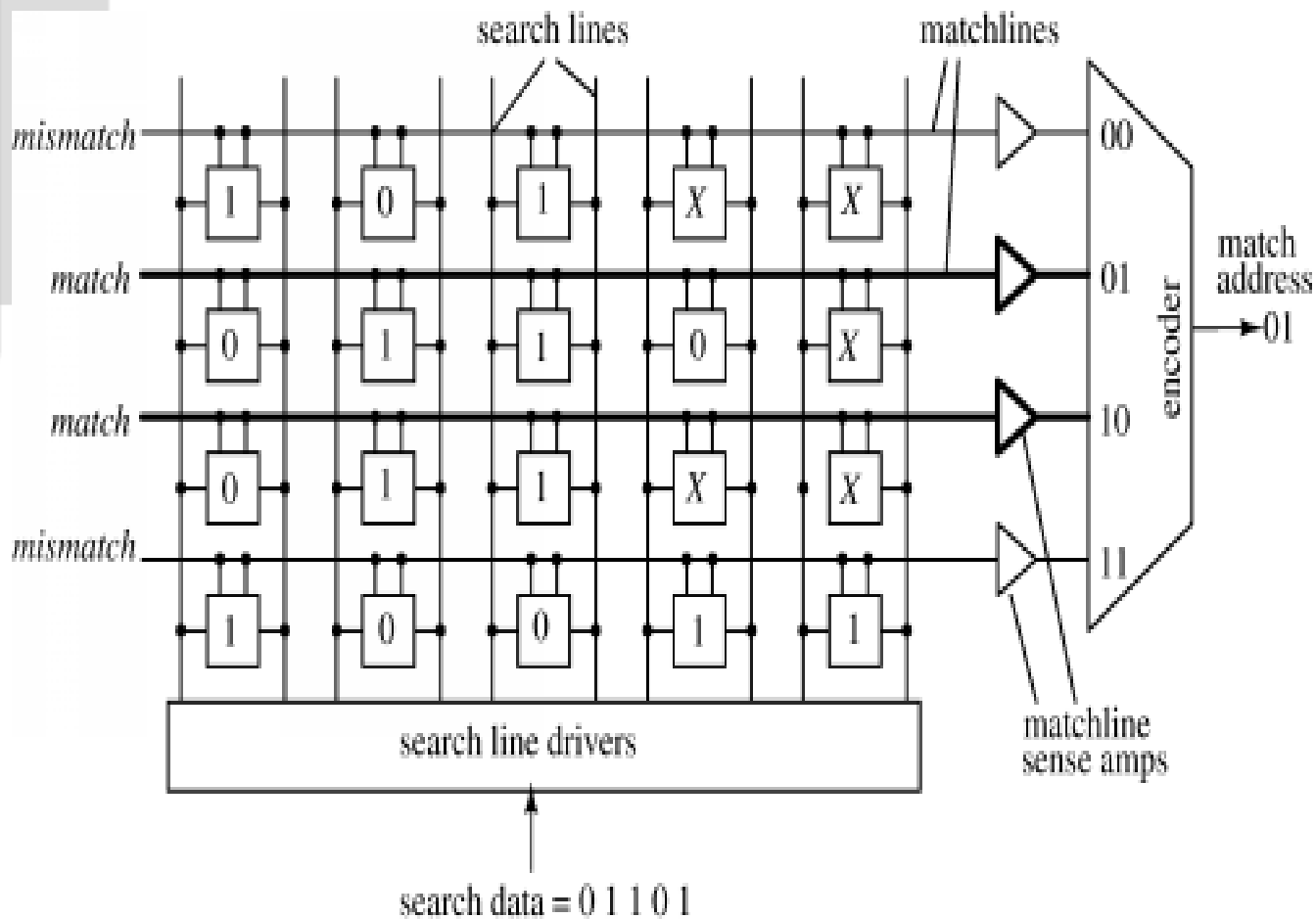
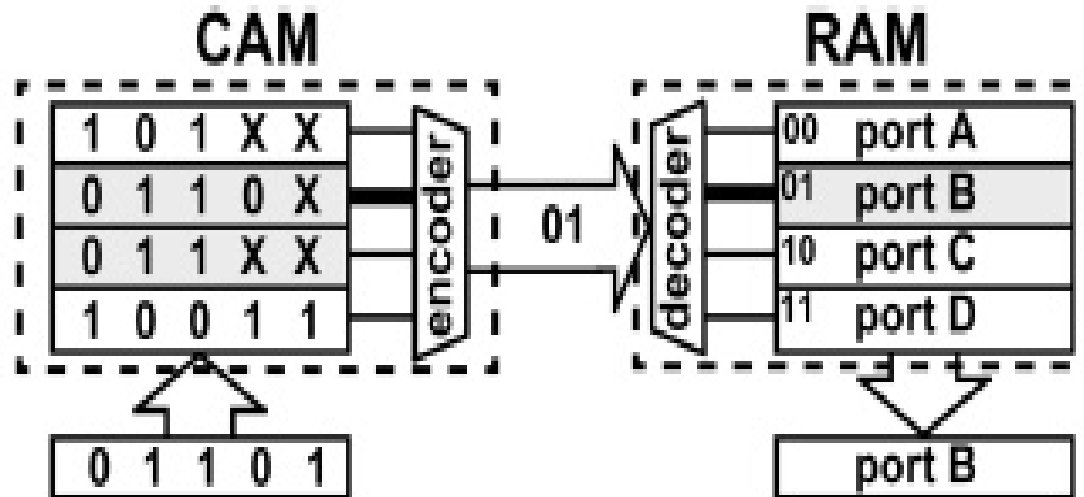
# CAM architecture


- When a line matches, we can output the address or location of that content
- When multiple entries match, output the first match
  - Gives priority to earlier entries



## Ternary CAM

- In many applications, we need to store Don't cares
- Three states: 0, 1, X
- Use two bits of actual storage to encode the three different values
- For example, use  $01 = 0$ ,  $10 = 1$ ,  $00 = X$

# TCAM Cell

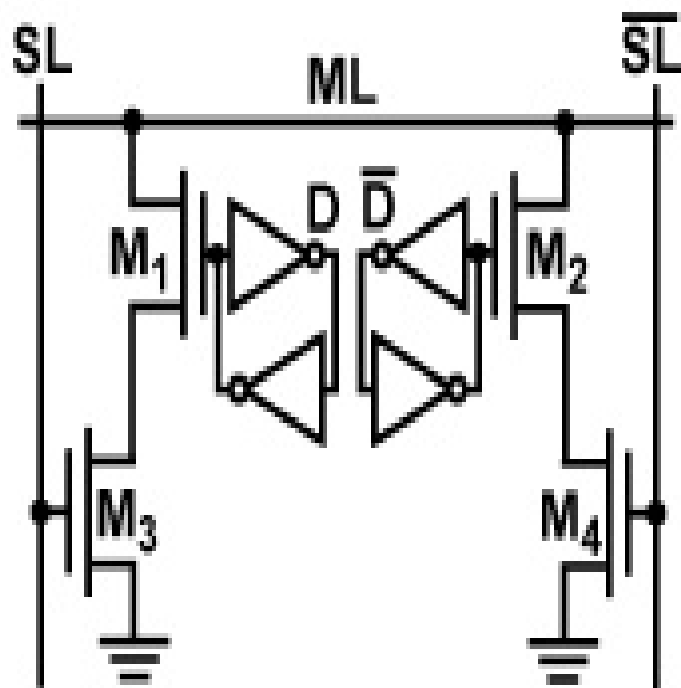

Stored Value	Stored		Search Bit	
	$D$	$\overline{D}$		
0	0	1	0	1
1	1	0	1	0
X	1	1	0	0

# TCAM

- Precharge Match line high
- When stored data matches search line –match line stays high
  - Otherwise, match line pulled low

## Persistent memory

- SRAM/DRAM lose memory when power is turned off
- More persistent memory needed for several applications
  - Photos in a digital camera
  - Bootable code or settings on circuits
- Flash memory used for these applications
  - Memory persists across power on/off cycles
  - Small size




# Flash memory


- Charge stored on an isolated conductor –called floating gate
- Charge has no path to dissipate
- The charge on the floating gate controls the current flowing between source and drain
  - Tells if a 1 or 0 is in the cell
- To erase the cell, a reverse voltage is applied between the drain and the controlling gate
  - Charge is dissipated through tunneling

# Flash Memory Cell
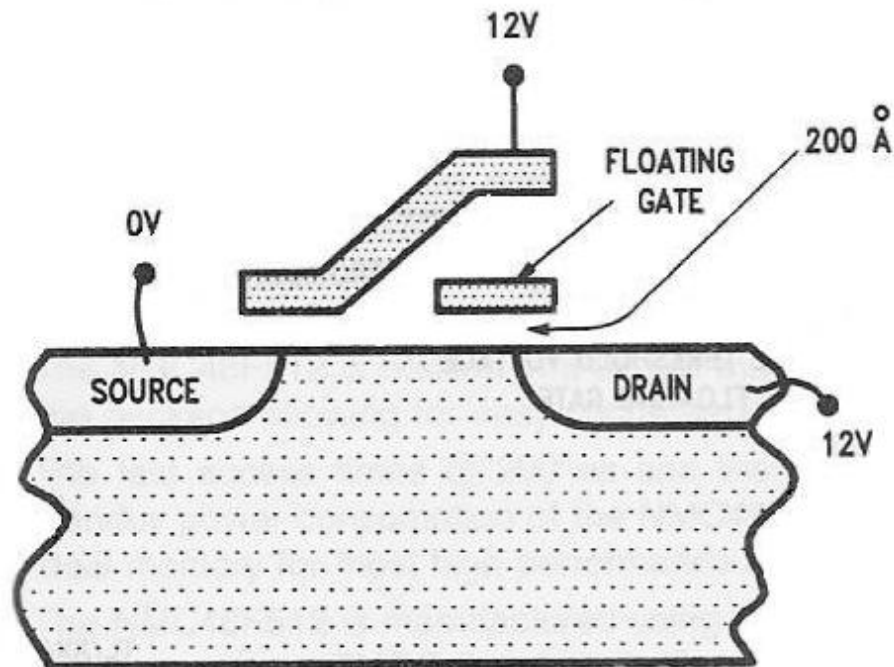
## Programming Via Hot Electron Injection




# Erasing Flash memory

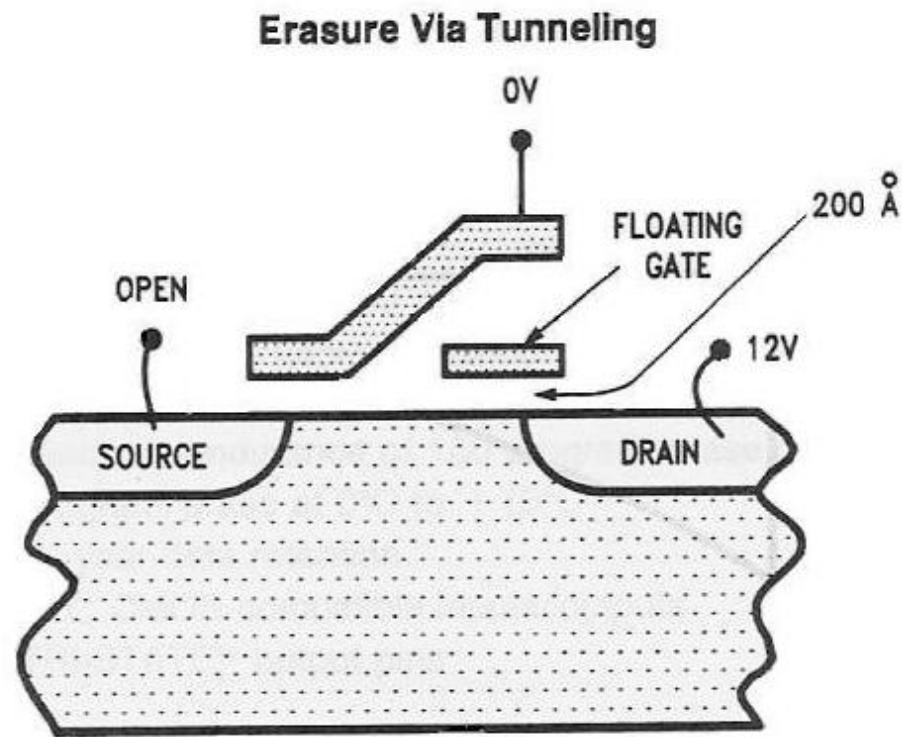

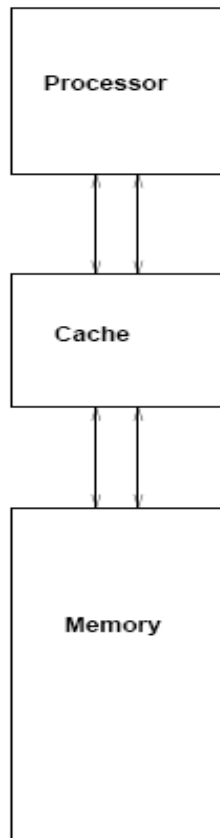
# Memory organizations


**Single word memory bus  
high bandwidth RAM**



**Wide memory bus**

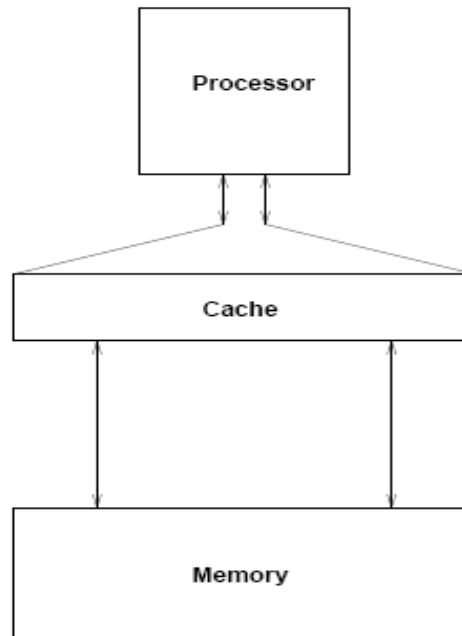


**Interleaved memory**

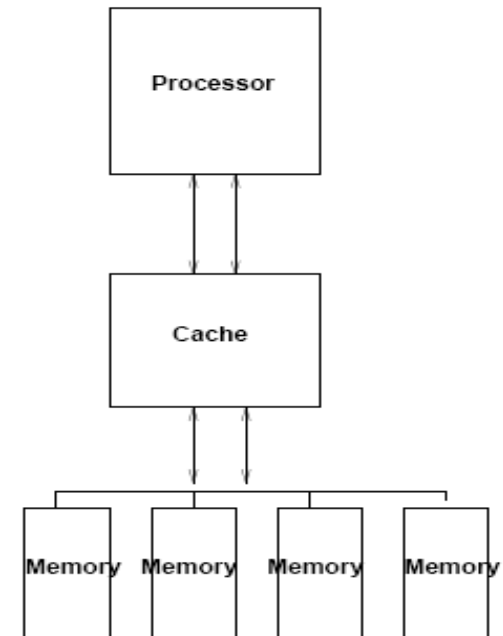

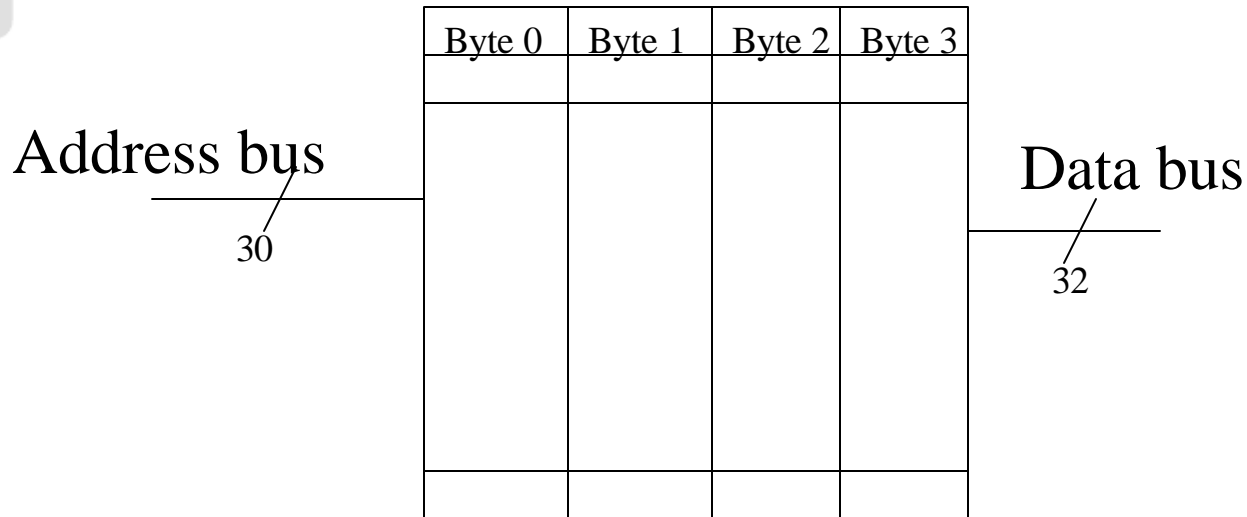
# Single word Memory Organization

- Word typically = 32 bits or 4 bytes
- Addresses normally for bytes
- $a_{31}a_{30}\dots a_2a_1a_0$  -- address bits  $a_1a_0$  not used when accessing memory



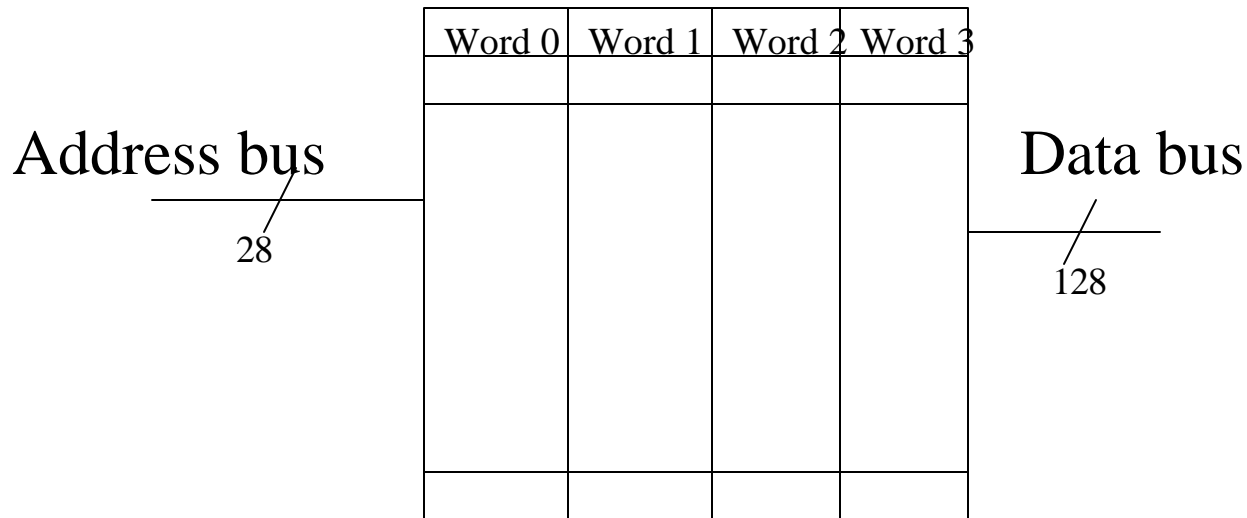
# Wide Memory Organization

- Memory is slow compared to cache/processor
- There is normally locality in memory accesses
  - If you access location A, likely to access A+1, A+2...
  - Why not access multiple words at a time to reduce access times


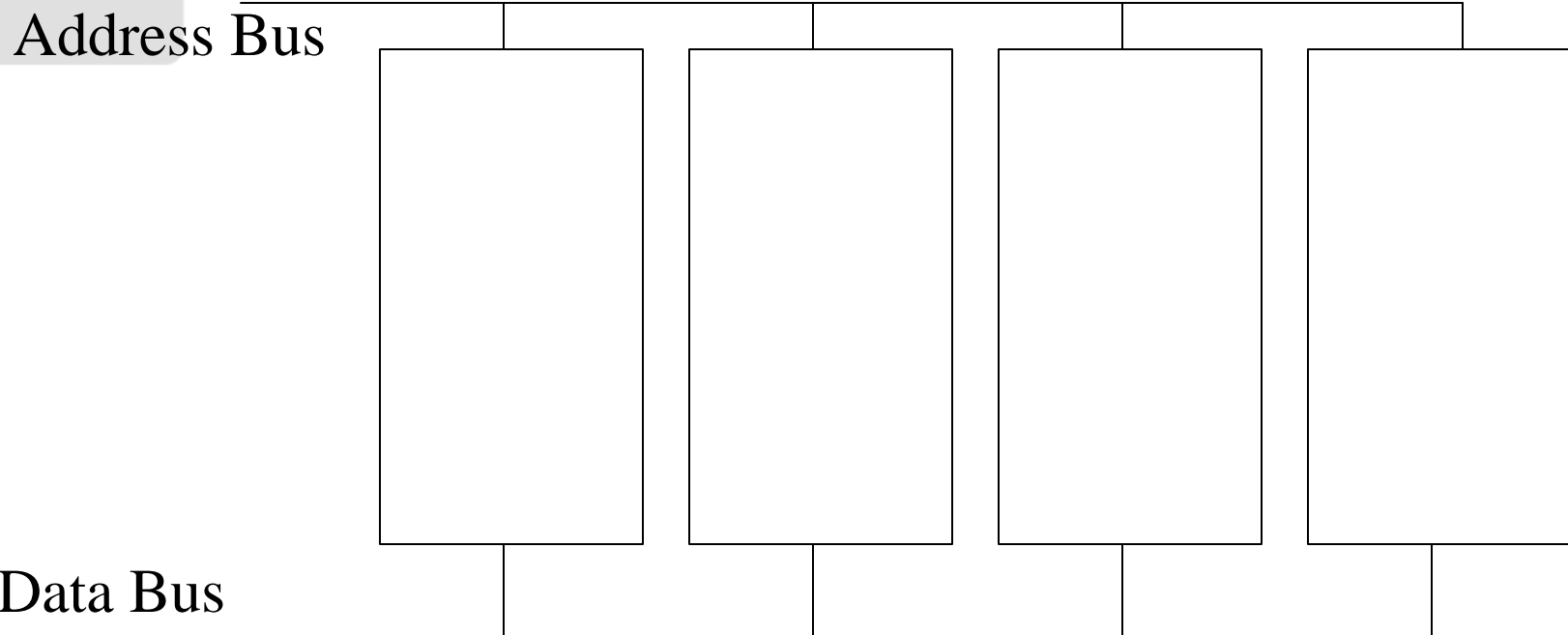
# Interleaved Memory Organization

- Organize memory into banks
- Each bank can be separately accessed
- Data is distributed across multiple banks to increase parallelism



# Interleaved Memory Organization

- Can keep multiple banks busy at the same time
- Give address to first bank, then a different address to second bank...so on
- Data accesses will be in different stages in different banks
- Somewhat like pipelined...
- Consider 4-bank memory with each bank organized as 2-word wide
- 3 bits  $a_2a_1a_0$  needed to address the 2-words (8 bytes)
- Each bank is addressed by the same  $a_4a_3$  bits. Bank 0 will have  $a_4a_3 = 00$ , bank 1 will have  $a_4a_3 = 11$ ....



# Interleaved Memory Organization

- Can function as a wide-word access if we give the consecutive addresses to different banks
- Can also access different words from different banks that are not consecutive
  - As long as there are no bank conflicts
- When will have bank conflicts in our example?
- Flash memories/drives have wide bank organizations
  - An example drive: with 2048 banks with each bank holding 512-byte sector
  - Access 1MB memory fast