

# Transmission Lines

---

- Outline
  - When to Invoke a Transmission Line Model
  - Equations for Propagation
  - Reflections

# When to Invoke a Transmission Line Model


---

- Suppose we have a wire. When is it to be viewed as a transmission line?
- **Short answer:** When the *time-of-flight* through the wire is comparable or larger than the rise/fall time of the source signal
- Time of flight is known if we know the velocity of wave propagation and the length of the wire. If the velocity of wave propagation is  $u$  and the length of the wire is  $l$ , then
$$u = \frac{l}{t}$$
- What if we need to model a wire as a transmission line?
  - We simply model the R/L/C of the wire in a **distributed** manner instead of a lumped manner.
  - This simply means using several  $\pi$  or  $T$  sections as appropriate (depending on the desired accuracy).
- OK, what about the long answer?
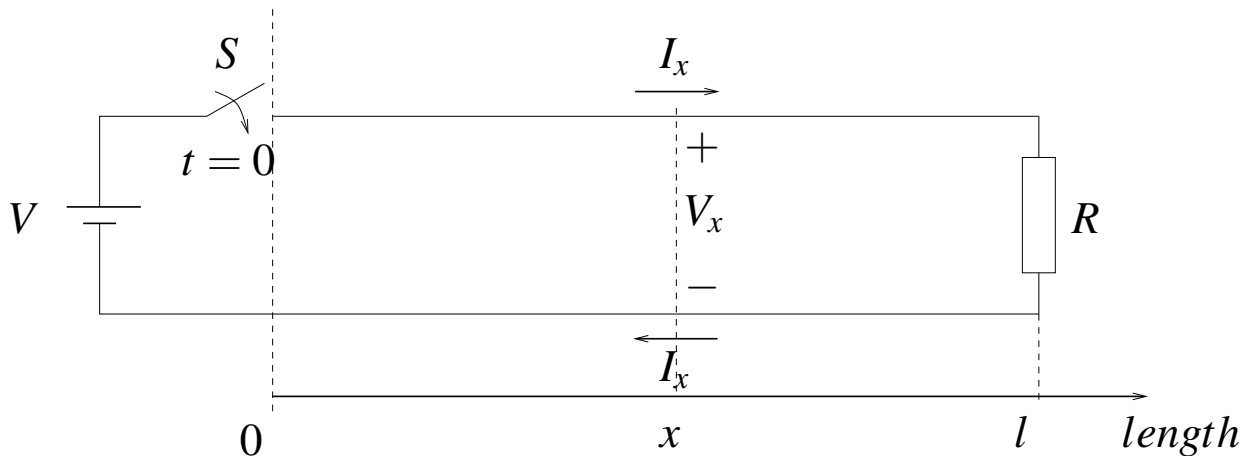
## Equations of Propagation

---





- Consider a wire of length  $l$ , connected to a voltage source  $V$ , and a switch  $S$  as shown below. The load resistance  $R$  is connected at the end of the wire.
- At time  $t = 0$ , the switch  $S$  is closed.



- The effect of closing  $S$  is not felt everywhere immediately
- Rather, this effect propagates from the source to load with a **finite** velocity
- Assuming uniform cross section, this velocity is given by  $u = \frac{1}{\sqrt{LC}}$ . Here  $u = \frac{c}{\sqrt{\kappa}}$ , where  $\kappa$  is the dielectric constant of the medium in which the wire resides.  $L$

and  $C$  are the inductance and capacitance per unit length of wire.

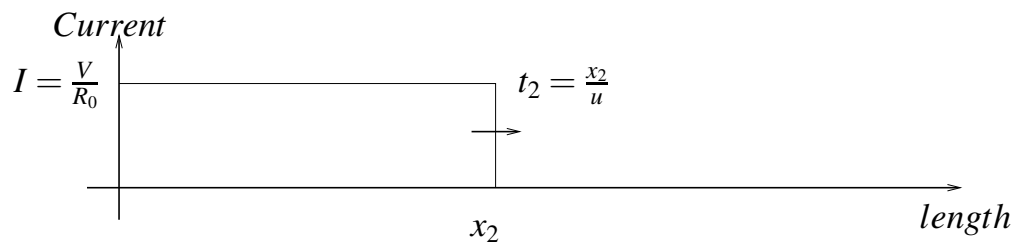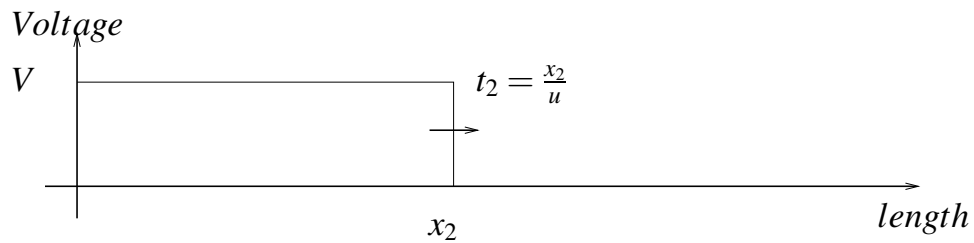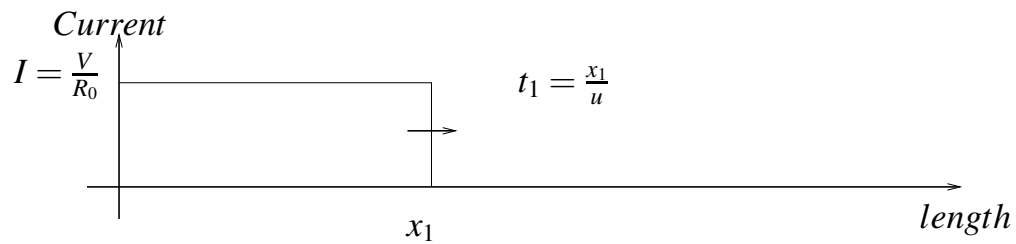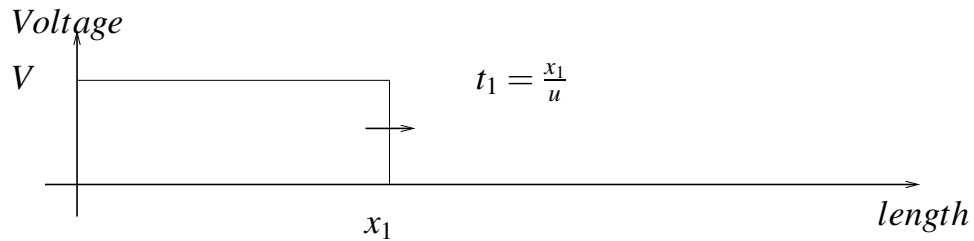- Note that if  $L$  increases,  $C$  decreases and vice versa.
- The voltage/current distributions on the wire at times  $t_1 = x_1/u$  and  $t_2 = x_2/u$  are shown below.



- We introduced a quantity  $R_0$  above. How is it computed and what is it? Lets explain this analytically
- At  $t_1$ , the voltage is  $V$  for  $0 \leq x \leq x_1$  and 0 for  $x_1 < x \leq l$
- In other words, a **front** of voltage travels to the right with velocity  $u$ .
- Lets say this front moves a distance  $dx$ . Then the capacitance to be charged is  $Cdx$  (since  $C$  is the capacitance per unit length)
- The charge required is  $dQ = VCdx$ . Hence the current is given by
- $$I = \frac{dQ}{dt} = VC \frac{dx}{dt} = VCu = VC \frac{1}{\sqrt{LC}} = V \sqrt{\frac{C}{L}} = \frac{V}{R_0}$$
- $R_0 = \sqrt{\frac{L}{C}}$  the **Characteristic Impedance** of the line.
- It is a function of the medium in which the wire resides. For PCBs,  $R_0$  is in the 50-75  $\Omega$  range.
- The expression for  $I$  above is the current for  $x = 0$  to wherever the front is. To the right of the front,  $I = 0$ .

- We say that  $I_x$  is positive when current flows to the right in the top wire, and to the left in the bottom wire.
- For all  $x$  from 0 to the location of the front (call it  $x$ ), we have  $V_x/I_x = R_0$ .
- If the source and load were interchanged, we would have  $V_x/I_x = -R_0$  based on our sign convention

# Reflections

---

- If the length  $l$  was infinite, then the front would keep moving to the right.
- If  $l$  is finite, then but if the load resistor  $R = R_0$ , then when the front arrives at the load (at time  $l/u$ ), currents at all points in the wire and the load are  $V/R_0$ , and so nothing further happens.
- It is as though the length  $l$  was infinite.
- Now lets suppose  $R \neq R_0$ . When the front arrives at the load (at time  $l/u$ ), the current in the wire is  $V_x/R_x = R_0$ . But **at the load**, the relationship  $V_l/R_l = R$  **is required**.
- This causes a discontinuity. Thus a **reflection** develops at the load, which moves to the left.
- The amplitude and polarity of this reflected wave are such that the **total** voltage  $V_l$  (i.e. sum of the incident and reflected voltage) is related to  $I_l$  by the expression  $V_l/I_l = R$
- If the incident voltage was  $V$ , the reflected voltage will be  $\rho V$  where  $\rho$  is the **reflection coefficient**

- If the incident current is  $V/R_0$ , reflected current is  $-\rho V/R_0$  based on our sign convention.
- The ratio of the total voltage to total current is  $R$ , therefore
 
$$R = \frac{V + \rho V}{V/R_0 - \rho V/R_0}.$$
- Solving, we get  $\rho = \frac{R/R_0 - 1}{R/R_0 + 1}$ . This reflection coefficient ranges from -1 to +1.
  - When  $R = R_0$ , then  $\rho = 0$ . So no reflections are observed (we agreed that should be the case above).
  - When  $R = \infty$  (i.e. the wire is **unterminated**),  $\rho = 1$
  - When  $R = 0$  (i.e. the wire is short-circuited),  $\rho = -1$
- There can be several reflections in this manner. We can compute the waveform at  $l$  by accounting for such reflections.



## Reflections - An Example

---

- Consider a wire of length  $l$ , with  $R_0 = 100\Omega$ ,  $R = 900\Omega$  and a source resistance  $R_s = 20\Omega$ . Also assume the source voltage is  $V = 12V$ . We want to determine the waveform at the end of the wire
- First we compute the reflection coefficients.
  - $\rho_R = \frac{\frac{900}{100} - 1}{\frac{900}{100} + 1} = 0.8$
  - $\rho_S = \frac{\frac{20}{100} - 1}{\frac{20}{100} + 1} = -0.75$
- A  $12V$  step appears on the line as a step of voltage  $V_1 = 12 \frac{R_0}{R_0 + R_s} = 10V$
- At time  $t = t_d = \frac{l}{u}$ , the wave  $V_1$  arrives at the end of the line, where it is reflected as:  
 $V_2 = \rho_R \cdot V_1 = 0.8 \cdot 10V = 8V$
- Therefore the receiver voltage at this time is  $V_1 + V_2 = 18V$
- At time  $2 \cdot t_d$ , the wave  $V_2$  arrives at the source. It is now reflected as:  
 $V_3 = \rho_S \cdot V_2 = -0.75 \cdot 8V = -6V$

- At time  $3 \cdot t_d$ , the wave  $V_3$  arrives at the end of the line. It is now reflected as:  

$$V_4 = \rho_R \cdot V_3 = 0.8 \cdot (-6)\text{V} = -4.8\text{V}.$$
- So the receiver voltage at this time is  $V_1 + V_2 + V_3 + V_4 = 7.2\text{V}$
- And so on...
- Asymptotically, the voltage at the end of the wire is  $V \cdot \frac{R}{R+R_s} = 12 \cdot \frac{900}{920} = 11.739\text{V}$ . The waveform at the end of the wire therefore looks like:

