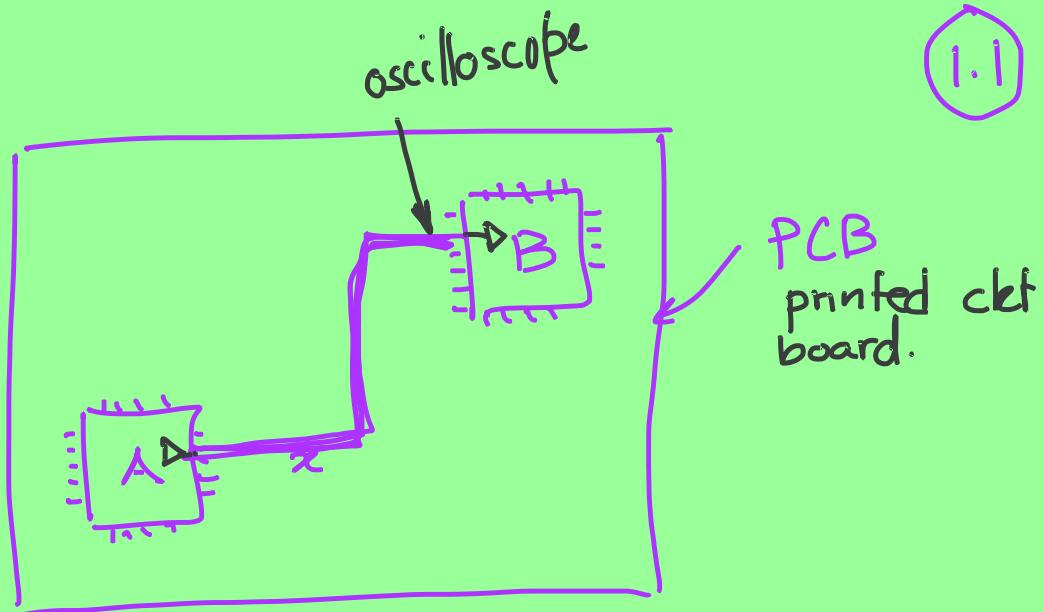



Transmission Lines

- Outline
 - When to Invoke a Transmission Line Model
 - Equations for Propagation
 - Reflections

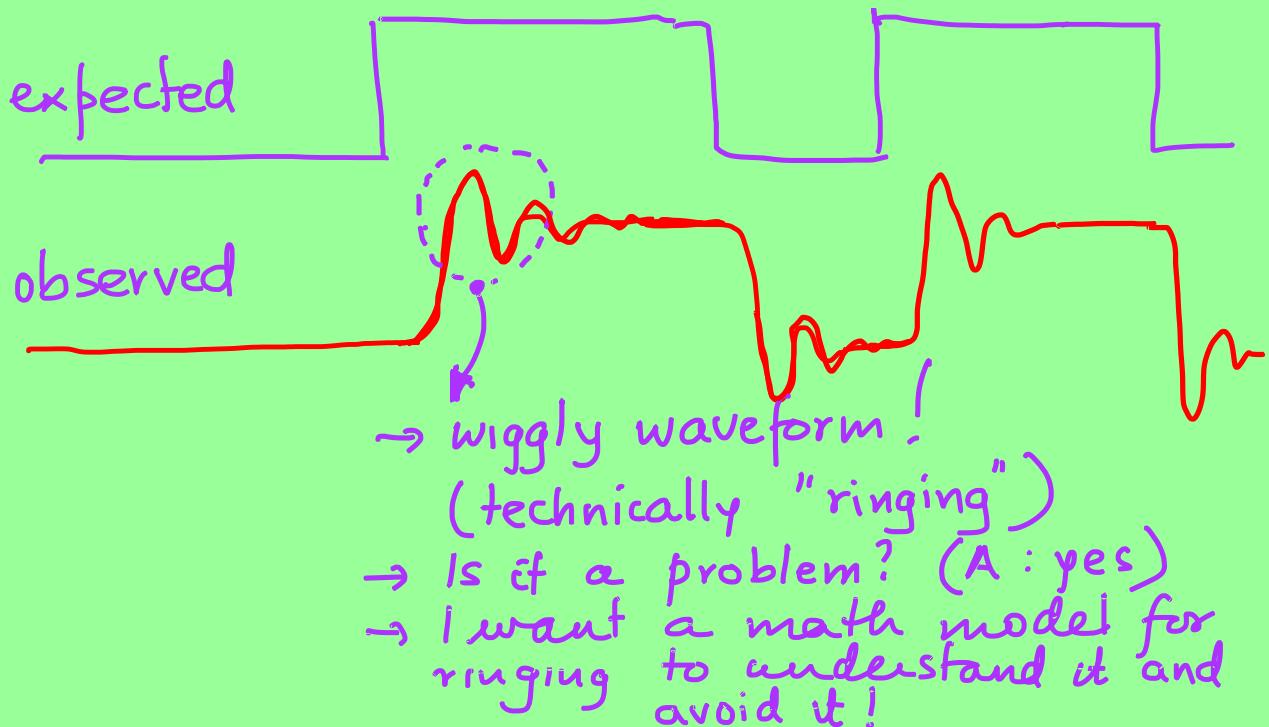1.1




- chip A drives a signal \underline{x} to chip B
- I probe signal \underline{x} at chip B.



(1.2)

Why is ringing a problem?

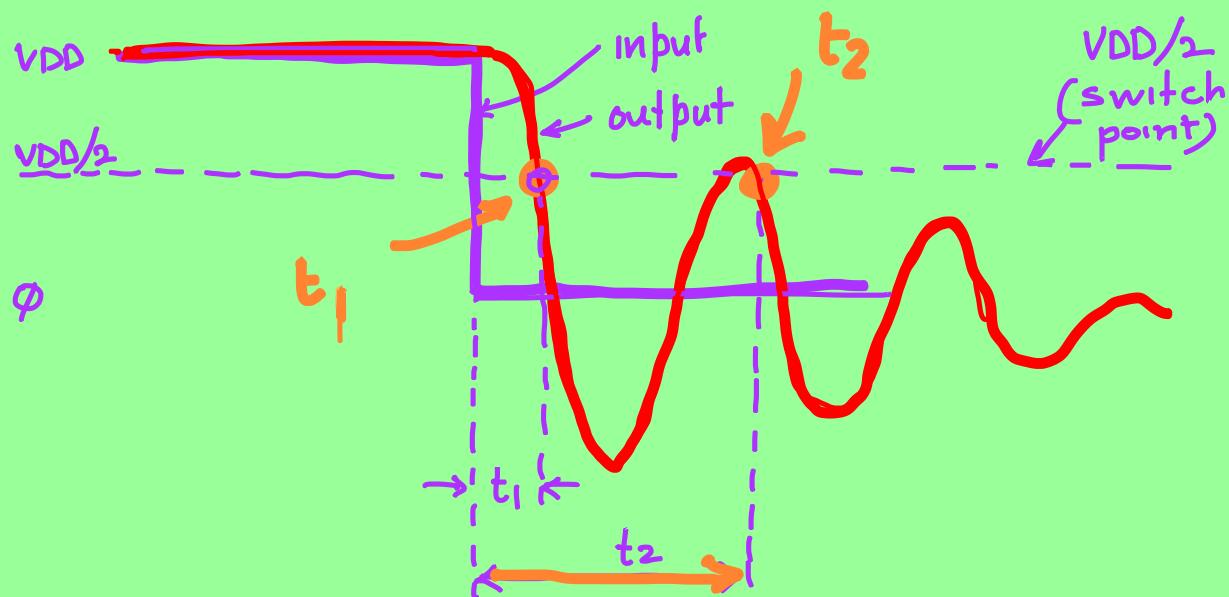

Without ringing \rightarrow delay is t_1


With ringing \rightarrow delay is $t_2 > t_1$ [NOT GOOD!]

How to a) model ringing in spice?

b) model ringing analytically
so we can control it?

a) How to model ringing? ^{in Spice}

(1.3)

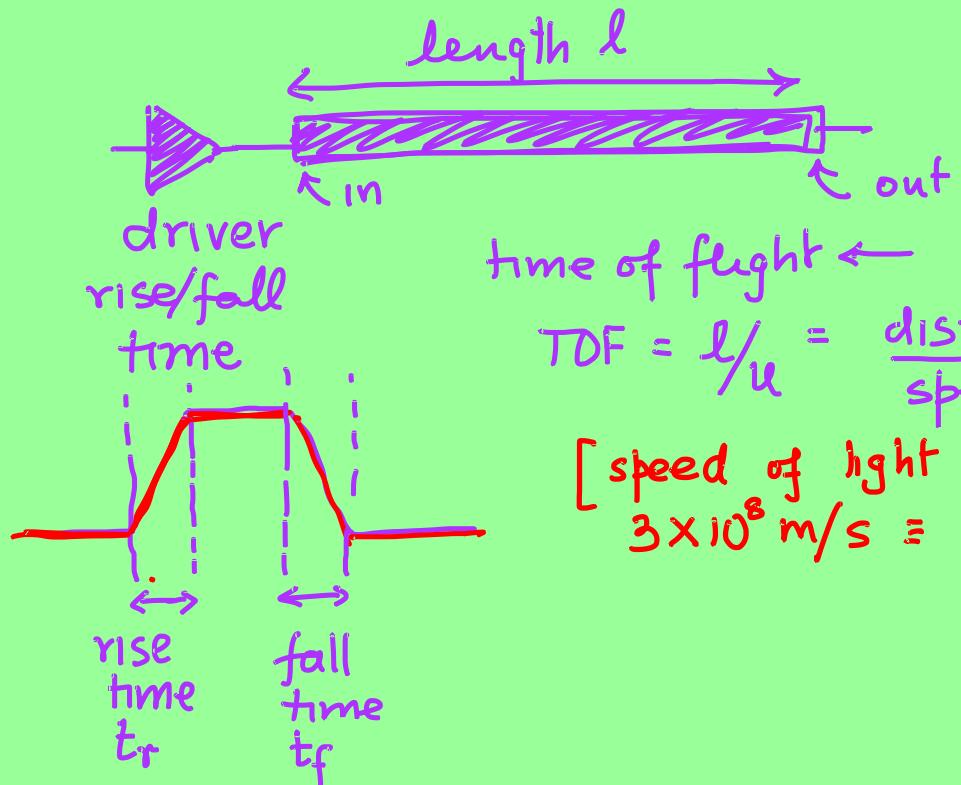

If in doubt
distribute

if $t_r (\approx t_f) \ll TDF$

we need to model ringing
(wire is treated as a
transmission line) "distributed"

else

we don't need to model "lumped"
ringing. Wire is not treated
as a transmission line

Lumped (no transmission line) 1.4

l, r, c are in a single "lump"



[Delay $\sim RC$] (estimate)

Distributed (transmission line)

l, r, c are "spread out" over the length of the wire




$\underbrace{\quad \quad \quad}_{\text{lots of}} \text{ little resistance/capacitance}$
whose total is r/c

[Delay $\sim RC/2$] (estimate)



How to model the wire as
a transmission line?

1.5

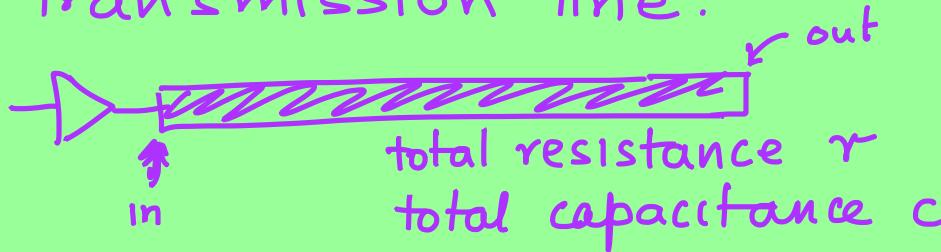

"Distribute" the r, c into T or Π

sections

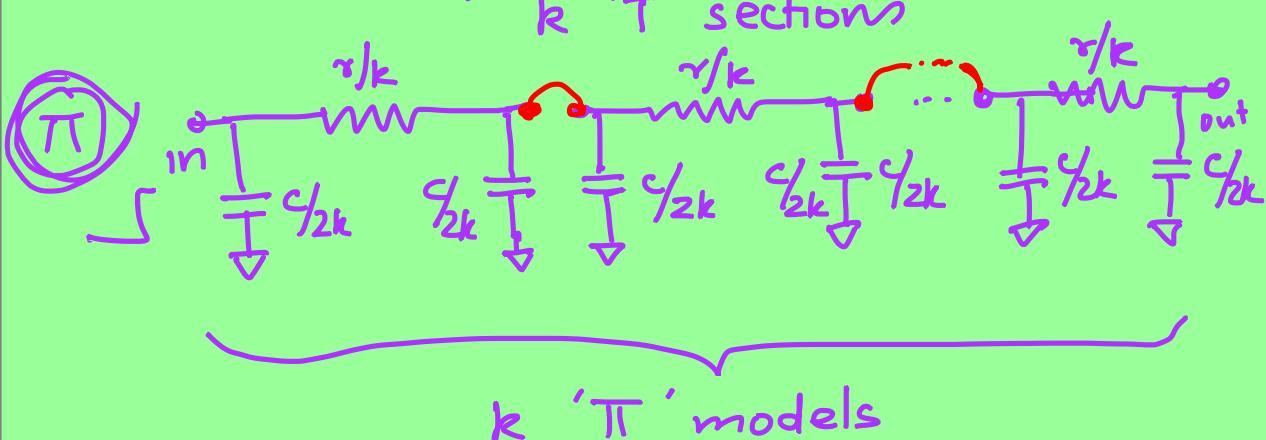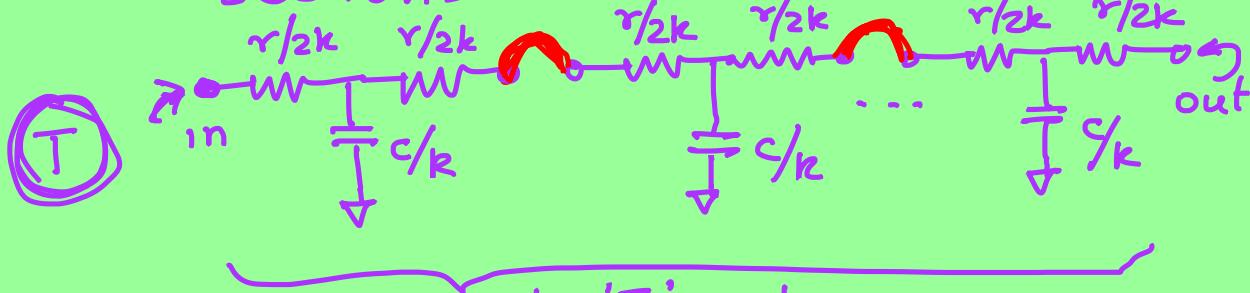

Q: Which one T or Π ?
A: either!

How many sections? ①.6

→ choose k experimentally

→ Try 1, 2, 3, 4... sections
and stop at a value


ST the delay difference
between $k-1$ and k
is within an error
tolerance that you
want.

When to Invoke a Transmission Line Model

- Suppose we have a wire. When is it to be viewed as a transmission line?
- **Short answer:** When the *time-of-flight* through the wire is comparable or larger than the rise/fall time of the source signal
- Time of flight is known if we know the velocity of wave propagation and the length of the wire. If the velocity of wave propagation is u and the length of the wire is l , then
$$u = \frac{l}{t}$$
- What if we need to model a wire as a transmission line?
 - We simply model the R/L/C of the wire in a **distributed** manner instead of a lumped manner.
 - This simply means using several π or T sections as appropriate (depending on the desired accuracy).
- OK, what about the long answer?

Equations of Propagation




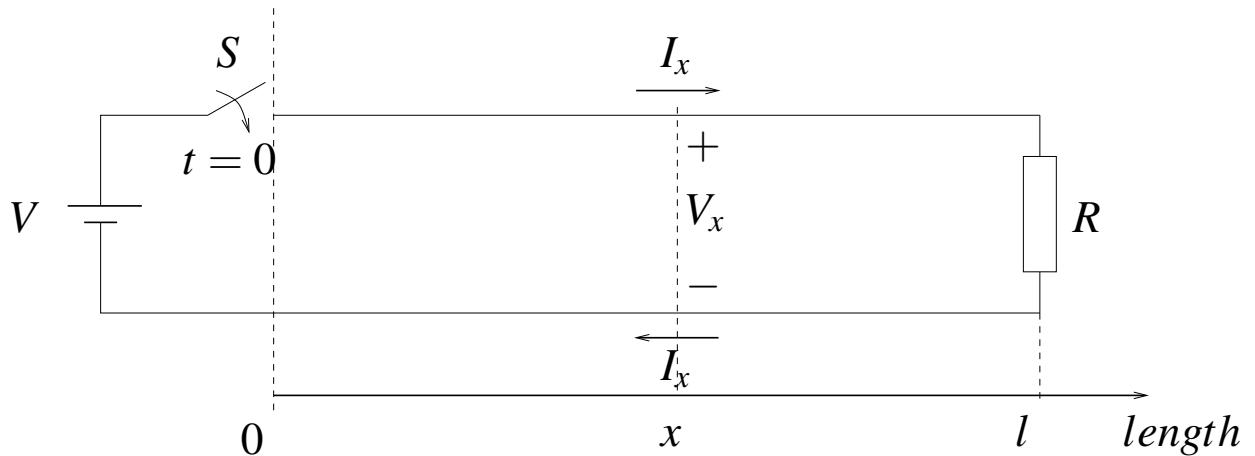
- Consider a wire of length l , connected to a voltage source V , and a switch S as shown below. The load resistance R is connected at the end of the wire.
- At time $t = 0$, the switch S is closed.



- The effect of closing S is not felt everywhere immediately
- Rather, this effect propagates from the source to load with a **finite** velocity
- Assuming uniform cross section, this velocity is given by $u = \frac{1}{\sqrt{LC}}$. Here $u = \frac{c}{\sqrt{\kappa}}$, where κ is the dielectric constant of the medium in which the wire resides. L

and C are the inductance and capacitance per unit length of wire.

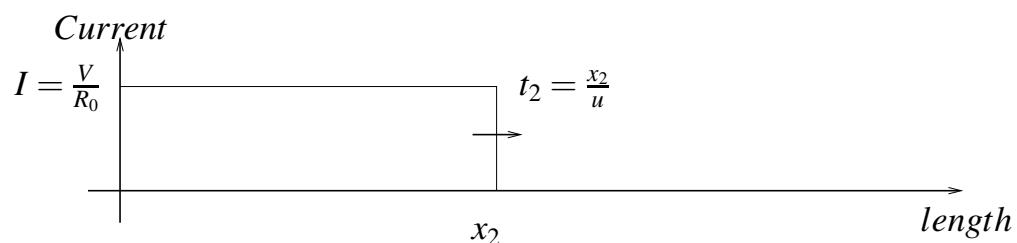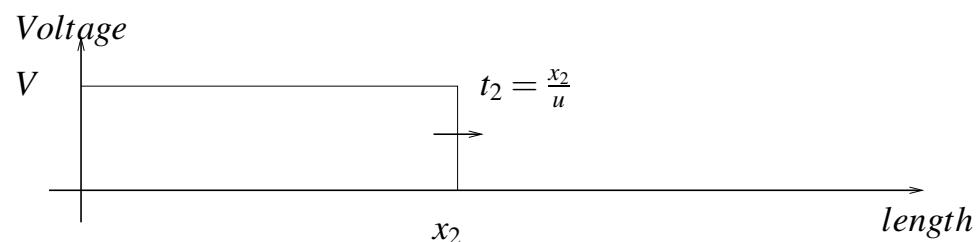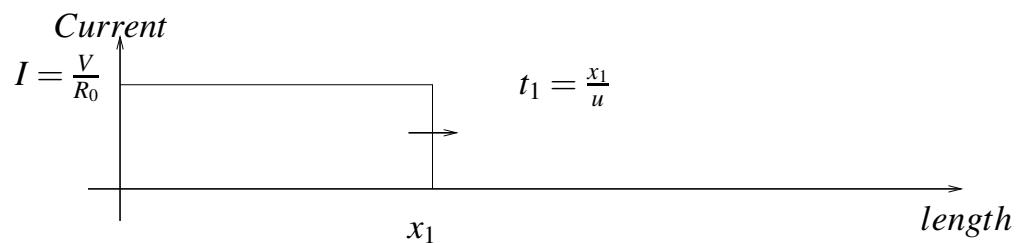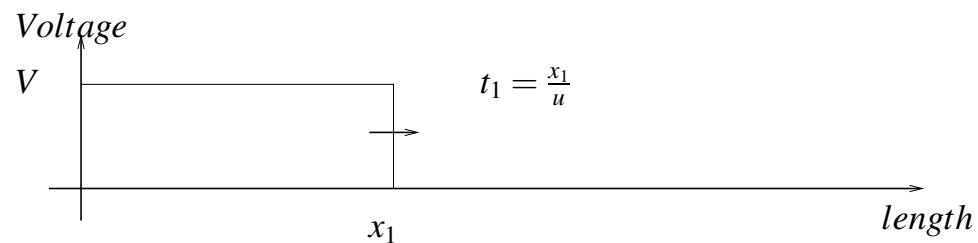
- Note that if L increases, C decreases and vice versa.
- The voltage/current distributions on the wire at times $t_1 = x_1/u$ and $t_2 = x_2/u$ are shown below.



- We introduced a quantity R_0 above. How is it computed and what is it? Lets explain this analytically
- At t_1 , the voltage is V for $0 \leq x \leq x_1$ and 0 for $x_1 < x \leq l$
- In other words, a **front** of voltage travels to the right with velocity u .
- Lets say this front moves a distance dx . Then the capacitance to be charged is Cdx (since C is the capacitance per unit length)
- The charge required is $dQ = VCdx$. Hence the current is given by
- $I = \frac{dQ}{dt} = VC \frac{dx}{dt} = VCu = VC \frac{1}{\sqrt{LC}} = V \sqrt{\frac{C}{L}} = \frac{V}{R_0}$
- $R_0 = \sqrt{\frac{L}{C}}$ the **Characteristic Impedance** of the line.
- It is a function of the medium in which the wire resides. For PCBs, R_0 is in the 50-75 Ω range.
- The expression for I above is the current for $x=0$ to wherever the front is. To the right of the front, $I=0$.

- We say that I_x is positive when current flows to the right in the top wire, and to the left in the bottom wire.
- For all x from 0 to the location of the front (call it x), we have $V_x/I_x = R_0$.
- If the source and load were interchanged, we would have $V_x/I_x = -R_0$ based on our sign convention

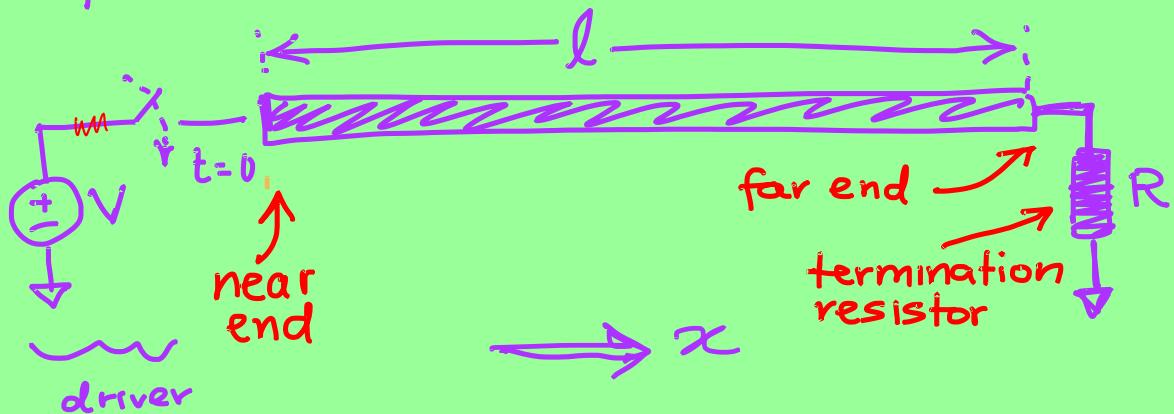b) Analytical model for transmission line:



$$\frac{\text{inductance}}{\text{length}} = L$$

$$\frac{\text{capacitance}}{\text{length}} = C$$

lowercase
c, speed
of light.
 $c = 3 \times 10^8 \text{ m/s}$


$$u = \frac{c}{\sqrt{L/C}} = \frac{1}{\sqrt{LC}} = \text{speed of wave}$$

dielectric
constant


$K \sim 4$ for most
PCB
PCB material is
called FR4

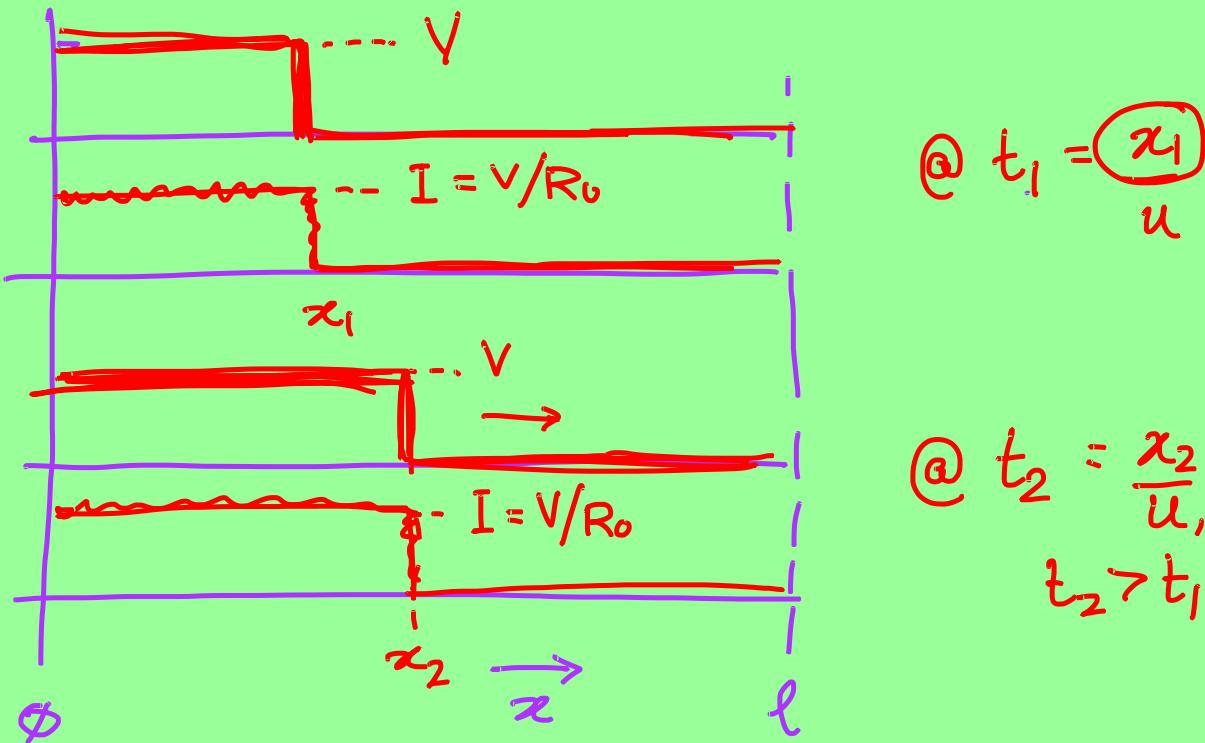(3.2)

- A wave of voltage (and current) moves from left to right



$\frac{V}{I} = R_0$ is a key (and non-intuitive)
quantity!
= characteristic impedance of wire
= Z_0

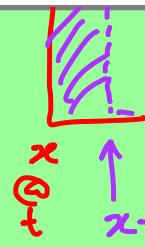Finding R_0 

(3.3)

→ Suppose wave has reached location x . at time t

→ In time \underline{dt} , it travels an extra distance dx

$$\frac{dx}{dt} = u = \frac{c}{\sqrt{K}} = \frac{1}{\sqrt{LC}}$$

from 3.1

→ In distance dx , the additional capacitance charged is $C \cdot dx$

→ Recall that $(Q = C \cdot V)$

charge = capacitance \times voltage

(3.4)

→ So the ^{electrical} charge needed to charge the additional capacitance $C \cdot dx$ from \emptyset to V volts is

$$\text{d}Q = (C \cdot dx) \cdot V$$

→ This is done in time dt . So

$$\frac{dQ}{dt} = C \cdot V \cdot \frac{dx}{dt}$$

$$I = C \cdot V \cdot u$$

$$\frac{I}{V} = C \cdot u = C \cdot \frac{1}{\sqrt{LC}} = \frac{I}{R_0}$$

$$R_0 = \sqrt{\frac{L}{C}}$$


(called characteristic impedance)

$$R_0 = 50-75 \Omega$$

3.5

R_o is NOT a physical resistance!! It just "springs into life" when there is a wave of V & I traveling in the wire, and it relates the V wave magnitude to the I wave magnitude

$$R_o = \frac{V}{I}$$

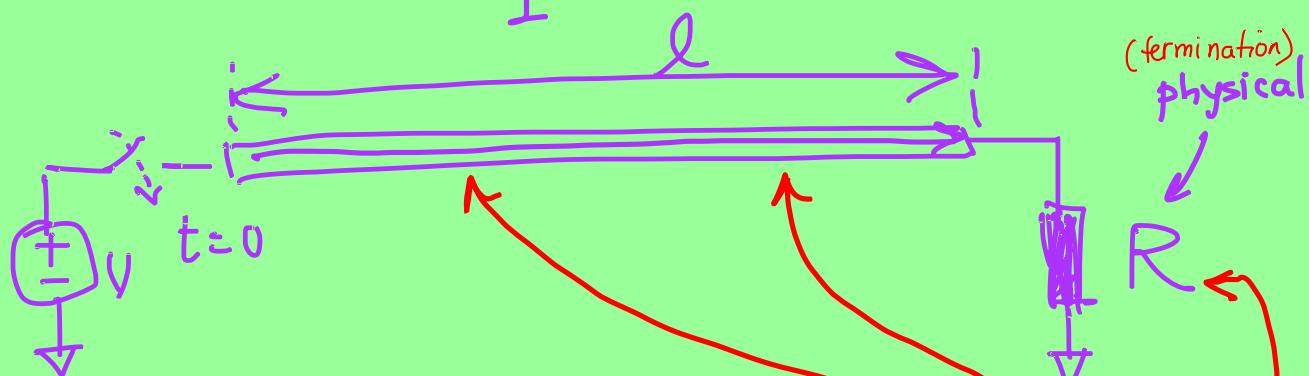

So when the wave is moving in the wire, $\frac{V}{I} = R_o$

But when the wave reaches the far end, we need $\frac{V}{I} = R$

WHAT IF $R \neq R_o$???

Reflections

- If the length l was infinite, then the front would keep moving to the right.
- If l is finite, then but if the load resistor $R = R_0$, then when the front arrives at the load (at time l/u), currents at all points in the wire and the load are V/R_0 , and so nothing further happens.
- It is as though the length l was infinite.
- Now lets suppose $R \neq R_0$. When the front arrives at the load (at time l/u), the current in the wire is $V_x/R_x = R_0$. But **at the load**, the relationship $V_l/R_l = R$ **is required**.
- This causes a discontinuity. Thus a **reflection** develops at the load, which moves to the left.
- The amplitude and polarity of this reflected wave are such that the **total** voltage V_l (i.e. sum of the incident and reflected voltage) is related to I_l by the expression $V_l/I_l = R$
- If the incident voltage was V , the reflected voltage will be ρV where **ρ is the reflection coefficient**

- If the incident current is V/R_0 , reflected current is $-\rho V/R_0$ based on our sign convention.
- The ratio of the total voltage to total current is R , therefore


$$R = \frac{V+\rho V}{V/R_0-\rho V/R_0}.$$
- Solving, we get $\rho = \frac{R/R_0 - 1}{R/R_0 + 1}$. This reflection coefficient ranges from -1 to $+1$.
 - When $R = R_0$, then $\rho = 0$. So no reflections are observed (we agreed that should be the case above).
 - When $R = \infty$ (i.e. the wire is **unterminated**), $\rho = 1$
 - When $R = 0$ (i.e. the wire is short-circuited), $\rho = -1$
- There can be several reflections in this manner. We can compute the waveform at l by accounting for such reflections.

Reflections - An Example

- Consider a wire of length l , with $R_0 = 100\Omega$, $R = 900\Omega$ and a source resistance $R_s = 20\Omega$. Also assume the source voltage is $V = 12V$. We want to determine the waveform at the end of the wire
- First we compute the reflection coefficients.
 - $\rho_R = \frac{\frac{900}{100} - 1}{\frac{900}{100} + 1} = 0.8$
 - $\rho_S = \frac{\frac{20}{100} - 1}{\frac{20}{100} + 1} = -0.75$
- A 12 V step appears on the line as a step of voltage $V_1 = 12 \cdot \frac{R_0}{R_0 + R_s} = 10V$
- At time $t = t_d = \frac{l}{u}$, the wave V_1 arrives at the end of the line, where it is reflected as:
 $V_2 = \rho_R \cdot V_1 = 0.8 \cdot 10V = 8V$
- Therefore the receiver voltage at this time is $V_1 + V_2 = 18V$
- At time $2 \cdot t_d$, the wave V_2 arrives at the source. It is now reflected as:
 $V_3 = \rho_S \cdot V_2 = -0.75 \cdot 8V = -6V$

- At time $3 \cdot t_d$, the wave V_3 arrives at the end of the line. It is now reflected as:
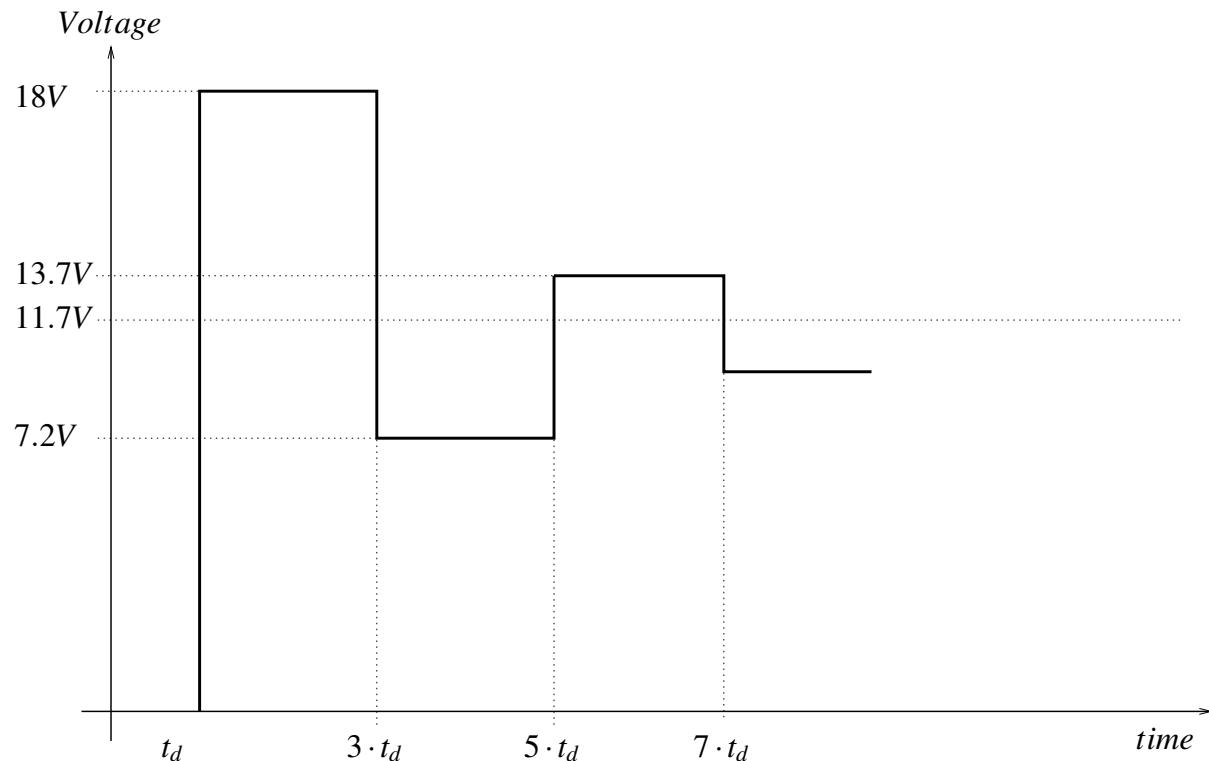
$$V_4 = \rho_R \cdot V_3 = 0.8 \cdot (-6)V = -4.8V.$$
- So the receiver voltage at this time is $V_1 + V_2 + V_3 + V_4 = 7.2V$
- And so on...
- Asymptotically, the voltage at the end of the wire is $V \cdot \frac{R}{R+R_s} = 12 \cdot \frac{900}{920} = 11.739V$ The waveform at the end of the wire therefore looks like:



when the wave reaches the far end.... 2 cases

4.1

(1) $R = R_0$

$$\frac{V}{I} \text{ along the wire} = R_0$$

$$\frac{V}{I} \text{ when wave reaches end} = R \\ (= R_0)$$

So it's like the wave kept on traveling... crisis averted!

(2) $R \neq R_0$

$$\frac{V}{I} \text{ along the wire} = R_0$$

$$\frac{V}{I} \text{ when wave reaches end} : R \neq R_0 \\ \underline{\text{CRISIS!!}}$$

→ Solution launch a reflected wave back towards the near end.

→ its voltage is $\ell \cdot V$ } so $\frac{\ell V}{R I} = R_0$ as $R I$ reqd.

→ its current is ℓI } (but its sign is -ve)

So, at far end : physical (terminating res.)

$$\frac{\text{total voltage}}{\text{total current}} = R = \frac{V + \ell V}{I - \ell I}$$

Massage the math:

(4.2)

$$\rho = \frac{R/R_0 - 1}{R/R_0 + 1}; \quad \rho \equiv \text{reflection coefficient}$$

NOTES • $-1 \leq \rho \leq 1$

- $R = R_0 \Rightarrow \rho = 0$

- $R = \infty \Rightarrow \rho = 1$ (open ckt-termination)

- $R = \emptyset \Rightarrow \rho = -1$ (short ckt-termination)


Reflected wave
if $\rho \cdot V = \emptyset \cdot V = \emptyset$.
(no reflection)
(matches intuition
of 4.1)

Reflected wave if
 $\rho V = -V$, so total
voltage @ far end is
 $V + \rho V = V - V = \emptyset$
(matches intuition)

Reflected wave if $\rho V = 1 \cdot V = V$.
So total voltage @ far end is
 $V + V = 2V$. OUCH. Can damage
far end chip input circuitry!


Workspace for 'transmission-lines'

Page 15 (row 3, column 9)

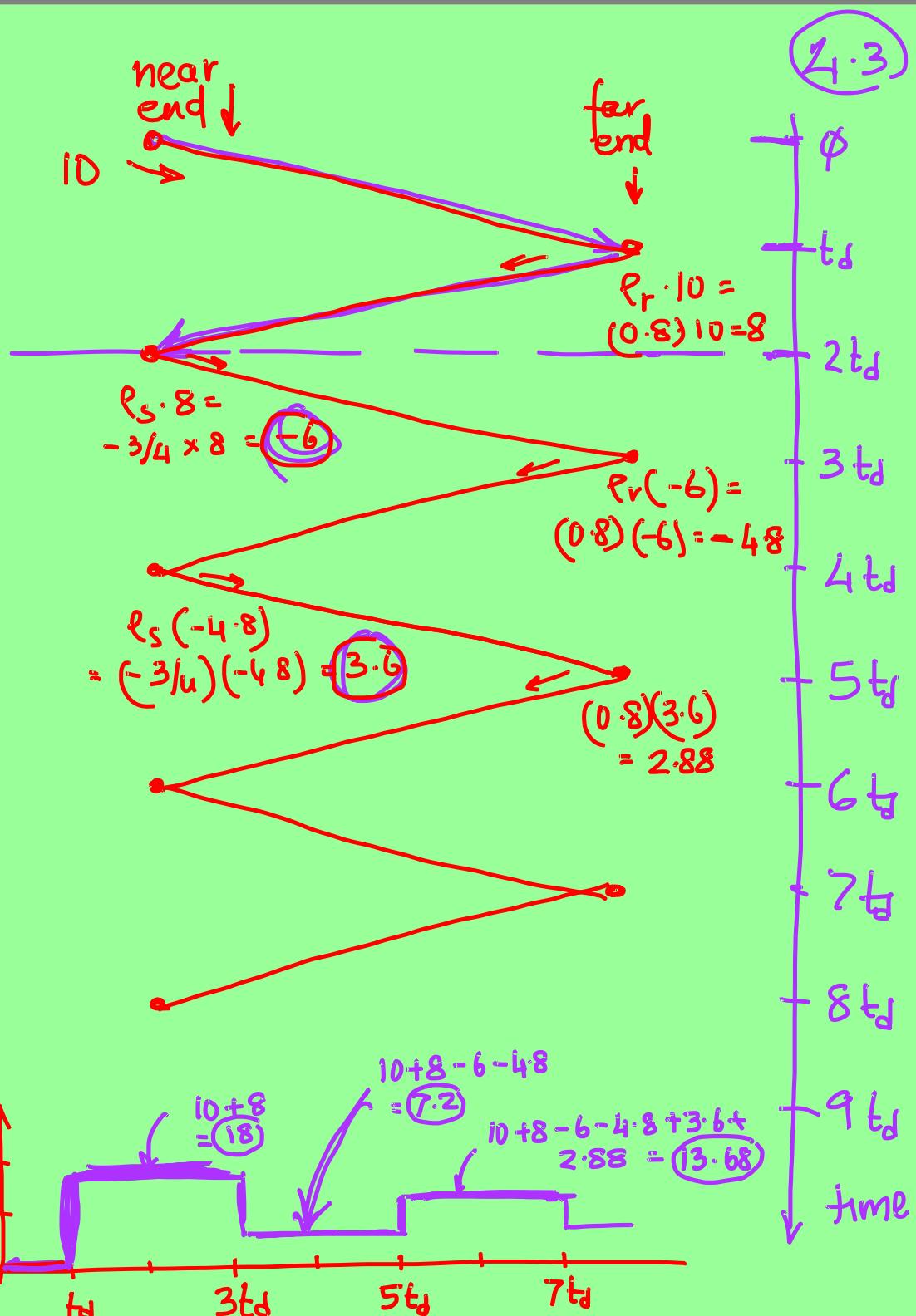

(4.4)

Far end voltage looks like

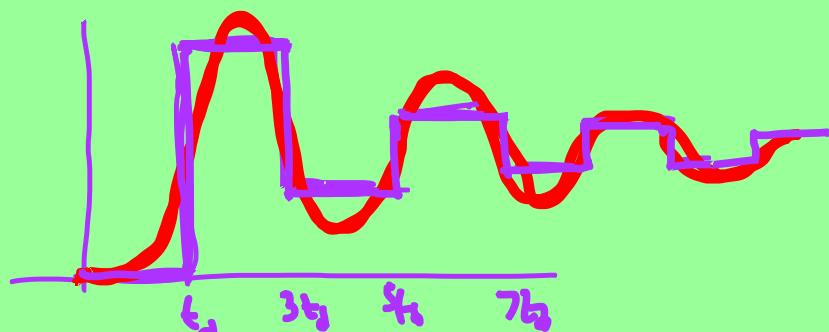

⊗ Just like the red waveform in 1.1 and 1.2 !!

⊗ if we want the voltage to never exceed X volts @ far end, just make sure that

$$V + \rho V = X$$

[if $R_o = 50\Omega$, $V = 2.5V$ and $X = 3V$, then]

$$2.5 + \rho(2.5) = 3$$

$$\rho = 0.2 = \frac{R/R_o - 1}{R/R_o + 1}$$

calc. R]

(4.5)

⊗ frequency of ringing ν

$$\left(\frac{1}{4L_d}\right) = \frac{1}{4(l/u)}$$

 l is wire length u is speed of wave (see 3.1)

OH - I
11/25/20

For no reflections }
(ie no ringing) } $R = R_o$

Problems w/ $R = R_o$

→ every PCB trace/wire needs
a resistor


✓ → expensive (\$)

✓ → expensive (pwr)

✓ → expensive (board area)

→ $R_o \sim 50\Omega$

$R = 50\Omega$ also

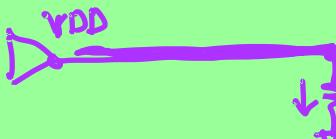 $i = \frac{V}{R} = \frac{V_{DD}}{50} = \frac{2.5V}{50}$ 50mA

$\left(\frac{50}{1000} \times 10000 \right) = 500A$

Workspace for 'transmission-lines'


Page 19 (row 3, column 13)

OH. 2

11/25/20

$$R = 200 \Omega \quad (R_0 = 50)$$
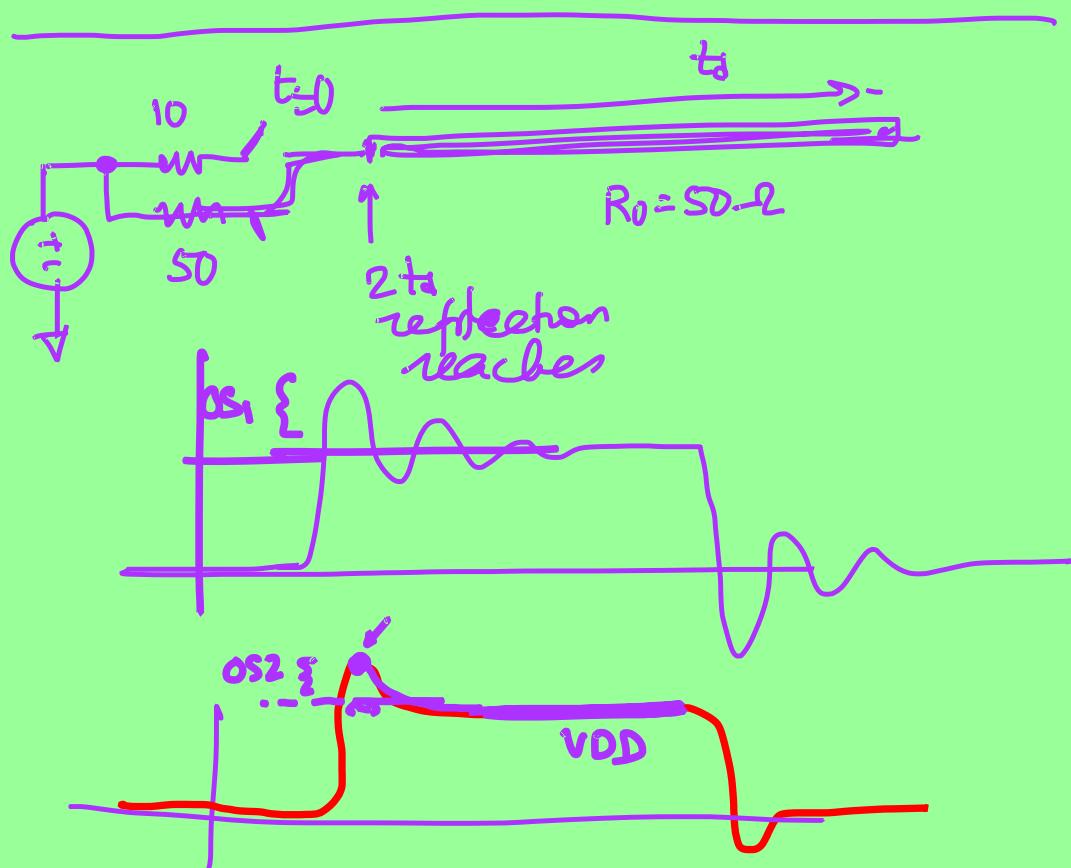
$$\rho = \frac{R/R_0 - 1}{R/R_0 + 1} = \frac{4 - 1}{4 + 1} = \frac{3}{5} = .6$$



Workspace for 'transmission-lines'

Page 21 (row 3, column 14)

