



**ELECTRICAL & COMPUTER  
ENGINEERING**  
TEXAS A&M UNIVERSITY

## Pre-Lab 3: Operational Amplifiers - Part 1

Kylan Lewis

UIN: 719001131

ECEN 325 -501

TA: Jian Shao

Date: 9/8/2020

## Calculations:

### 1. Solution:

Read the datasheet for the UA741 opamp and write down the typical values of the following parameters:

**Supply Voltage:**  $\pm 5\text{ V}$  (Min)  $\pm 15\text{ V}$  (Max)

**Power Consumption:** 85 mW (Average)

**Input Resistance:**  $0.3\text{ M}\Omega$

**Input Offset Voltage:** 1mV-6mV; 7.5mV (@ Full range)

**Output Resistance:**  $75\ \Omega$  (Average)

**Input Offset Current:** 200 nA (Average); 300nA (@ Full range)

**Voltage Gain:** 106.02 dB open loop at 2K load

**Bandwidth:** .7MHz - 1 MHz GBP

**Slew Rate:**  $0.5\text{ V}/\mu\text{s}$

\*Average = (25 degrees Celsius)

Derive the voltage gains  $\frac{V_{o1}}{V_i}$ ,  $\frac{V_{o2}}{V_i}$ , and  $\frac{V_{o3}}{V_i}$  for the circuits in Fig. 1, assume the opamps are ideal.

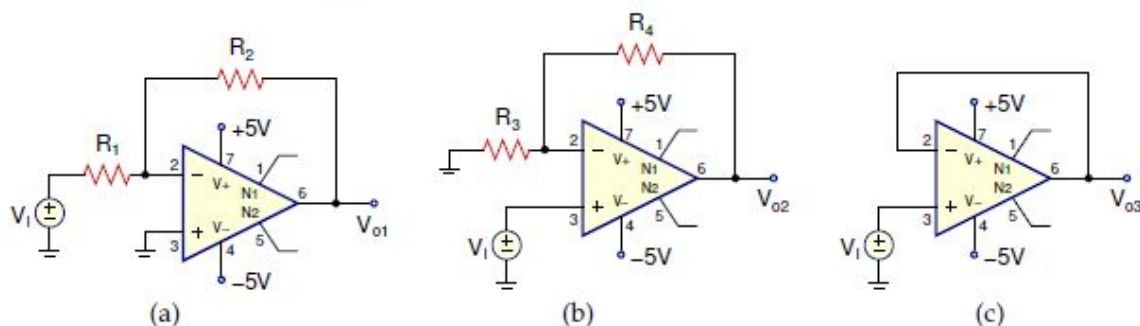


Figure 1: Opamp configurations (a) Inverting amplifier (b) Non-inverting amplifier (c) Voltage follower

## 2. Calculations

a.

$$V_X = 0, I_1 = I_2, \text{ No input current}$$

$$\frac{V_I - V_x}{R_1} = \frac{V_x - V_{o1}}{R_2} ; \frac{V_{o1}}{V_I} = \frac{-R_2}{R_1}$$

b.

$$V_y = V_I, I_1 = I_2, \text{ No input current}$$

$$\frac{0 - V_y}{R_3} = \frac{V_I - V_{o2}}{R_4} ; \frac{-V_I}{R_3} = \frac{V_I - V_{o2}}{R_4}$$

$$\frac{V_{o2}}{R_4} = \frac{V_I}{R_4} + \frac{V_I}{R_3} ; \frac{V_{o2}}{V_I} = \left( 1 + \frac{R_4}{R_3} \right)$$

c.

$$\text{Output voltage} = \text{Input voltage}$$

$$V_{o3} = V_I$$

## 3. Calculations

$$R_1 = R_3 = 10 \text{ k}\Omega, \frac{V_{o1}}{V_I} = -3, \frac{V_{o2}}{V_I} = 6$$


$$\frac{V_{o1}}{V_I} = -3 ; \frac{-R_2}{R_1} V_I = -3$$

$$R_2 = 3R_1 ; R_2 = 30 \text{ k}\Omega$$

$$\frac{V_{o2}}{V_I} = 6 ; \left( 1 + \frac{R_4}{R_3} \right) = 6$$

$$\frac{R_4}{R_3} = 5 ; R_4 = 5(R_3) ; R_4 = 50 \text{ k}\Omega$$

# Circuit Design:

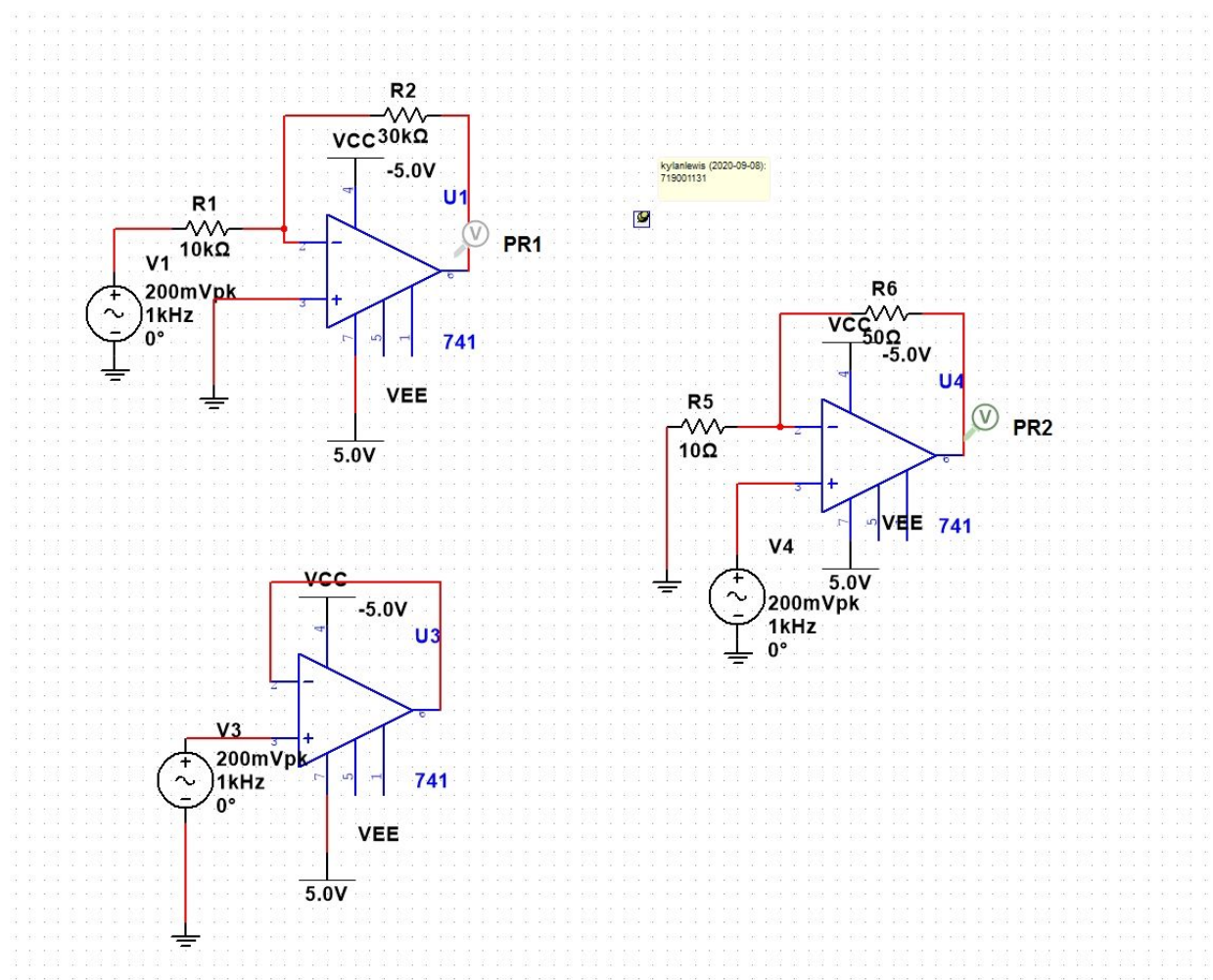

## Breadboard:

