



**ELECTRICAL & COMPUTER
ENGINEERING**
TEXAS A&M UNIVERSITY

Post-Lab 4: Operational Amplifiers

Part 2

Kylan Lewis

UIN: 719001131


ECEN 325 -501

TA: Jian Shao


Date: 9/16/2020

Schematics:


Summing Amplifier Schematic

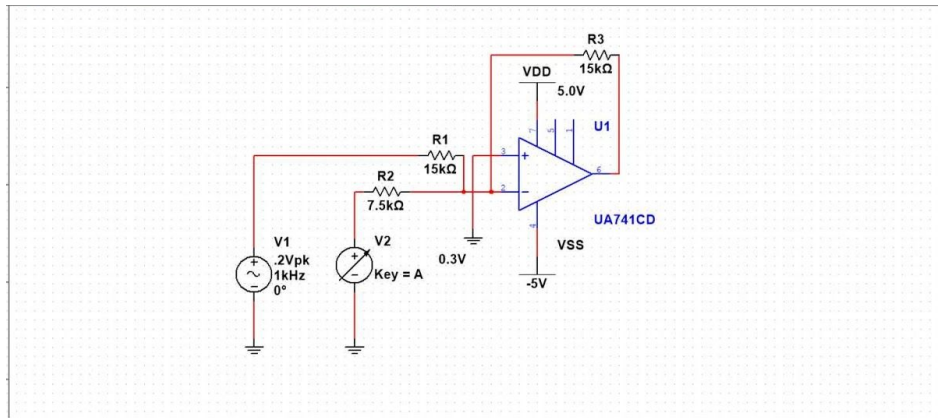

Differential Amplifier Schematic

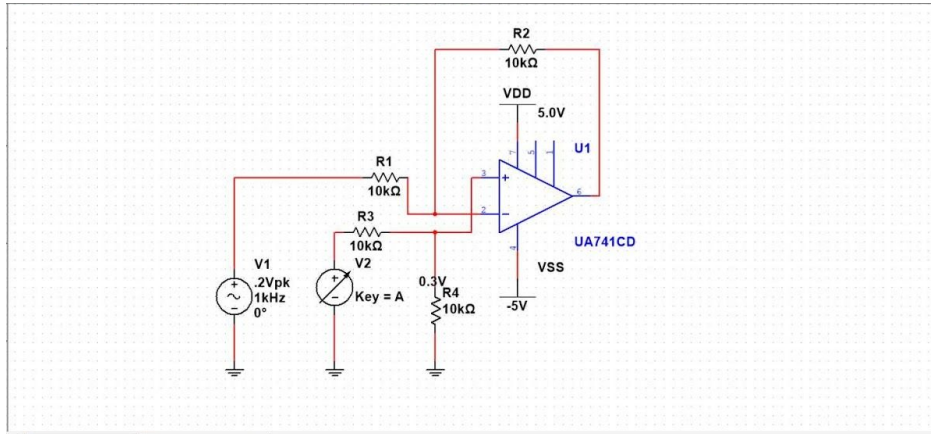


Instrumentation Amplifier Schematic

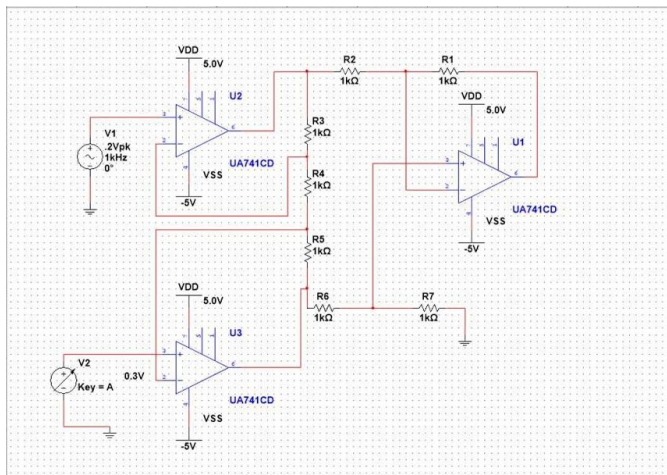


Simulations:

1.) Apply the inputs $V_{i1} = 0.2 \sin(2\pi 1000t)$ and $V_{i2} = 0.3V$, and obtain the time-domain waveforms


Summing Amplifier

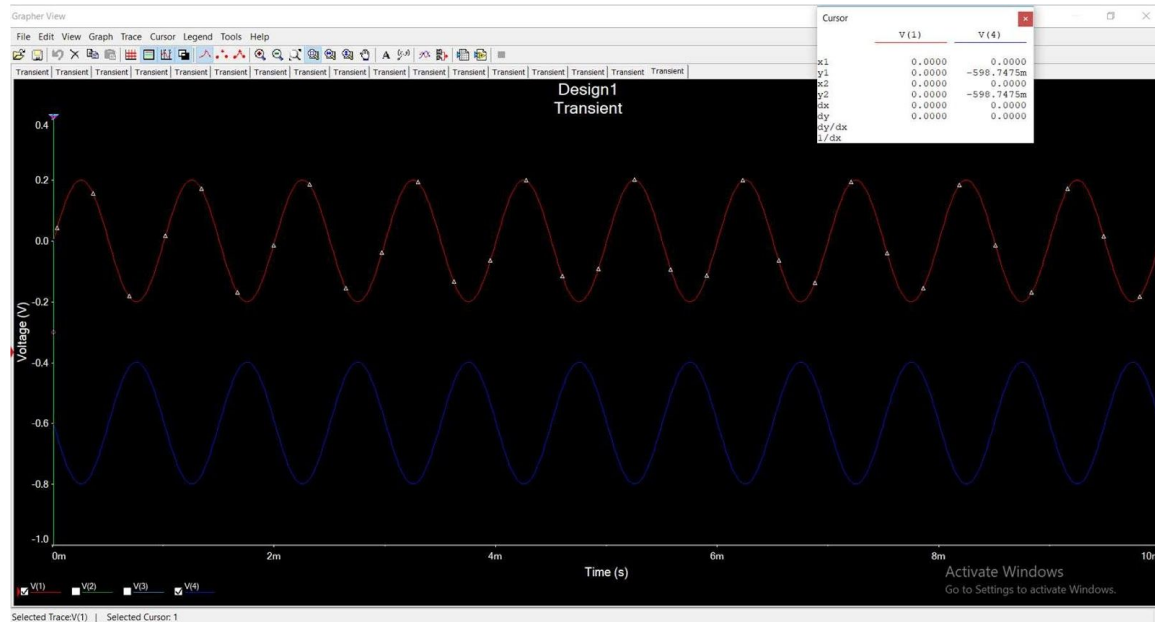

Differential Amplifier

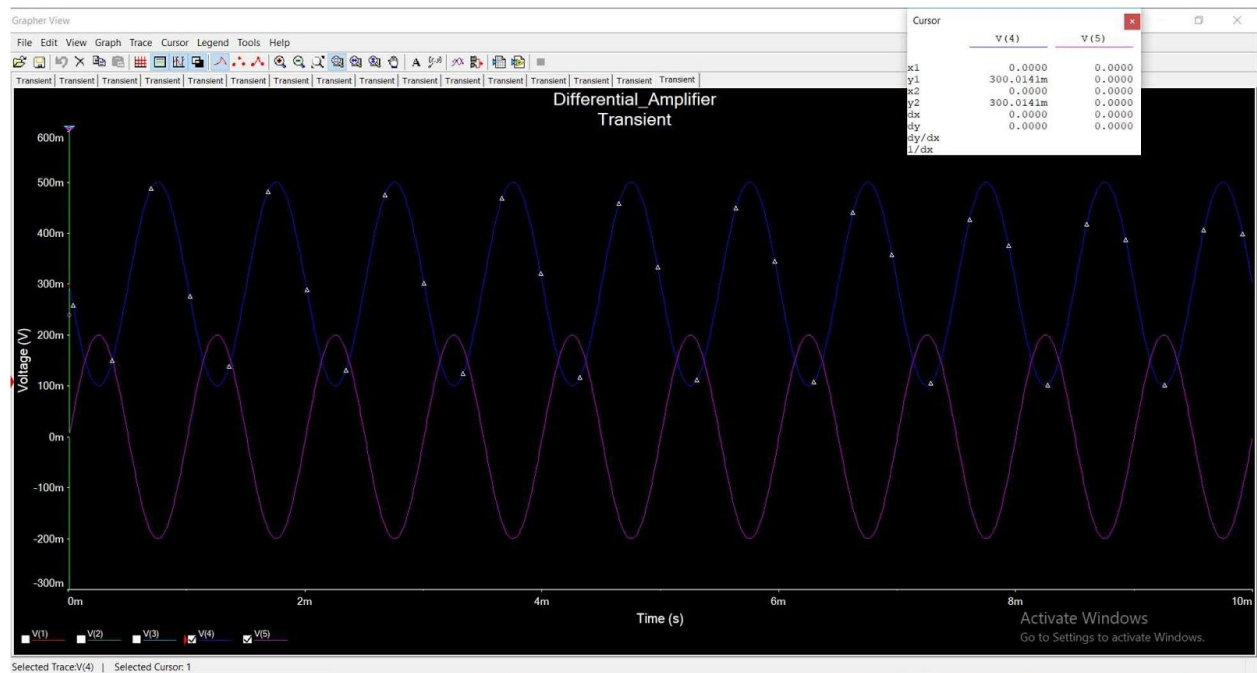

Instrumentation Amplifier

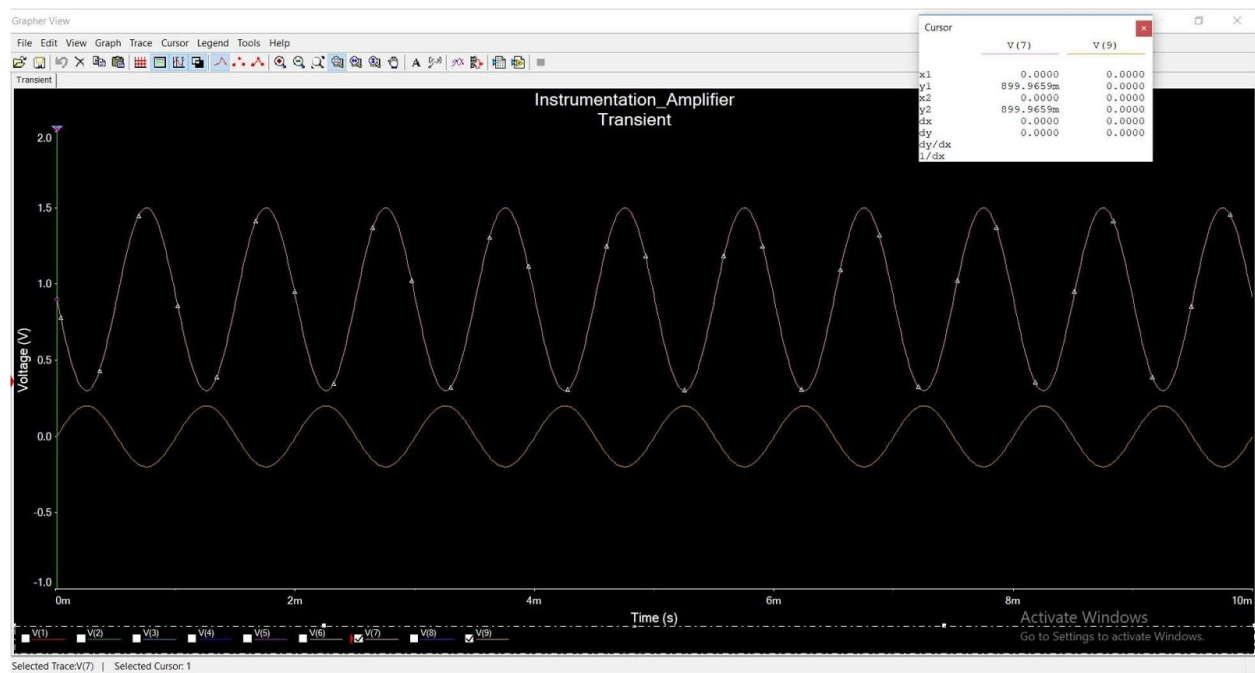

TA Question:

(between 7:00 and 17:00) is,

Ideally for the differential amplifier, if the two inputs are the same, the output should be zero. However, in the video, the output still shows a peak-peak value of 3mV. Why do you think this may happen?

This phenomenon is known as the Common Mode Output Voltage and is usually less than the input voltage. Basically the 3mV is the unwanted voltage (noise) in the system that is common to both the input terminals. This occurs because our models are ideal and we are not predicting any other factors. Things that can cause this noise include; offset signal in the driver circuit, ground differentials, and radiated signals.