



**ELECTRICAL & COMPUTER  
ENGINEERING**  
TEXAS A&M UNIVERSITY

## Post-Lab 3: Operational Amplifiers - Part 1

Kylan Lewis


UIN: 719001131

ECEN 325 -501


TA: Jian Shao

Date: 9/9/2020


## Simulations:


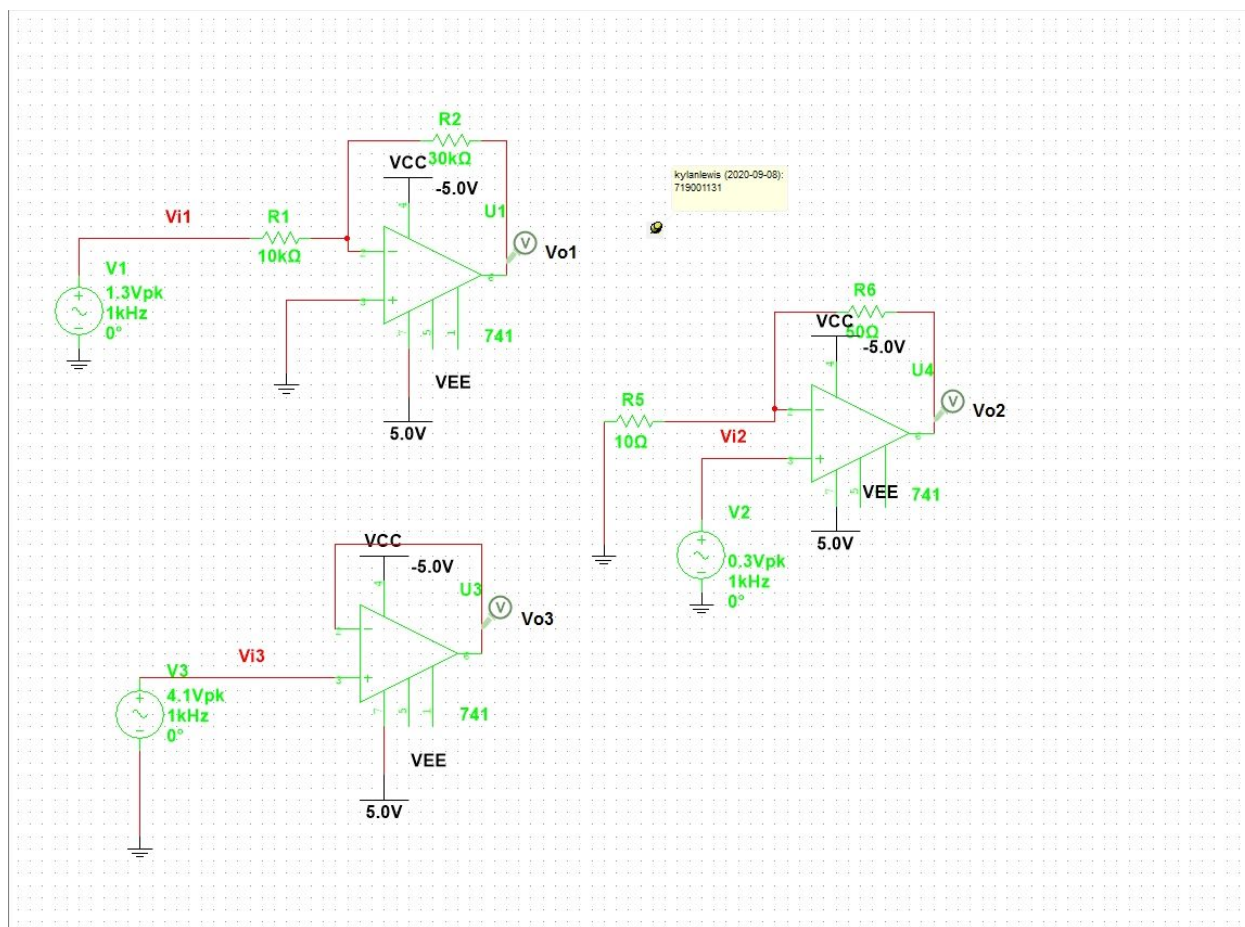


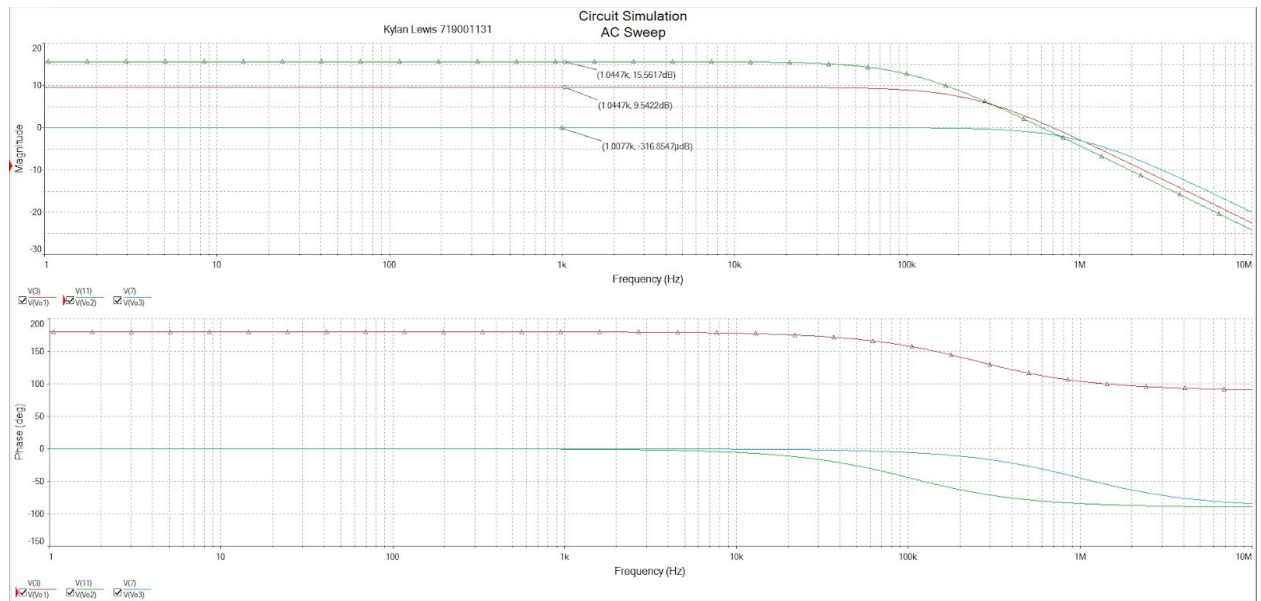1. Bode Plot using AC simulation (gain measured @ 1 kHz)





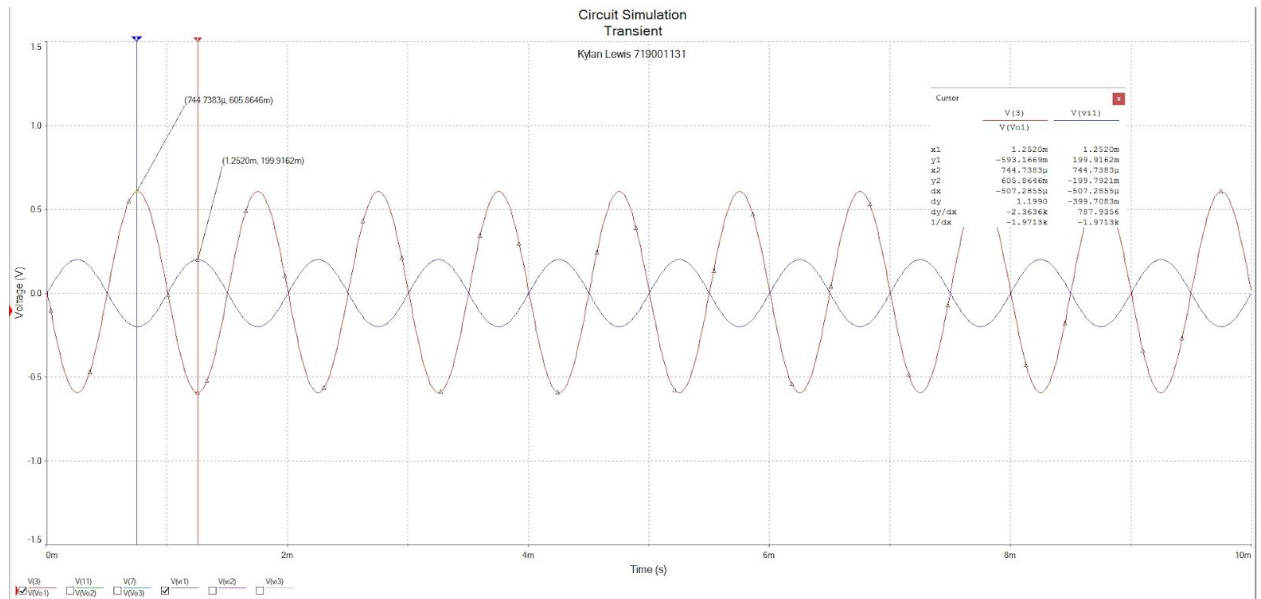
2.  $V_i(t) = 0.2\sin(2\pi 1000t)$  using Transient



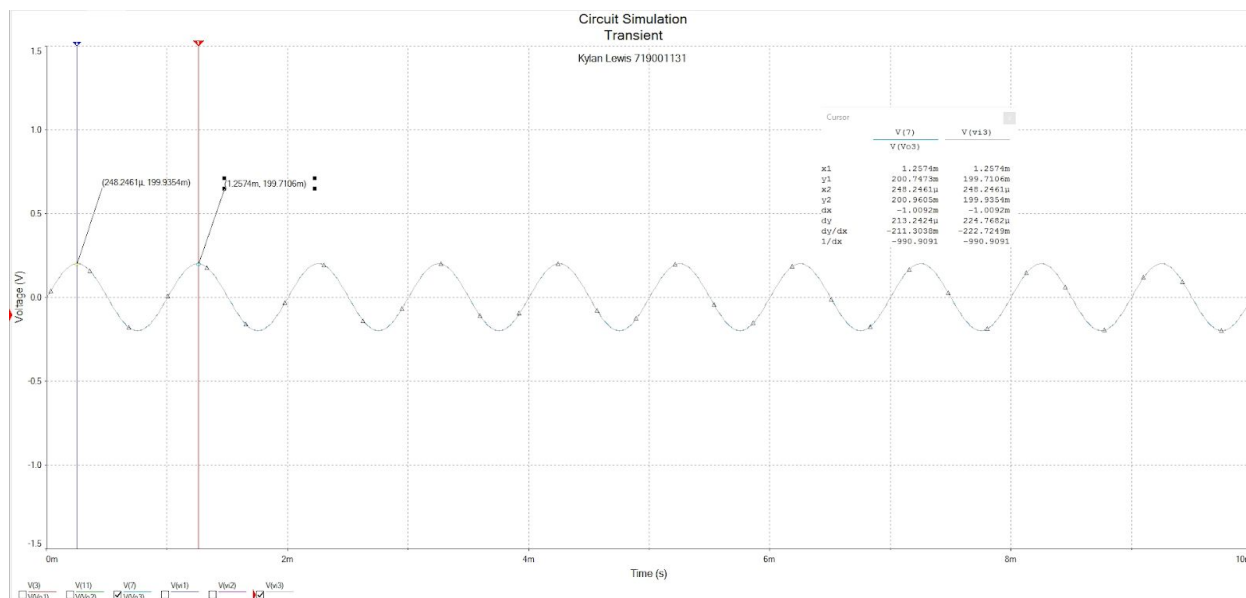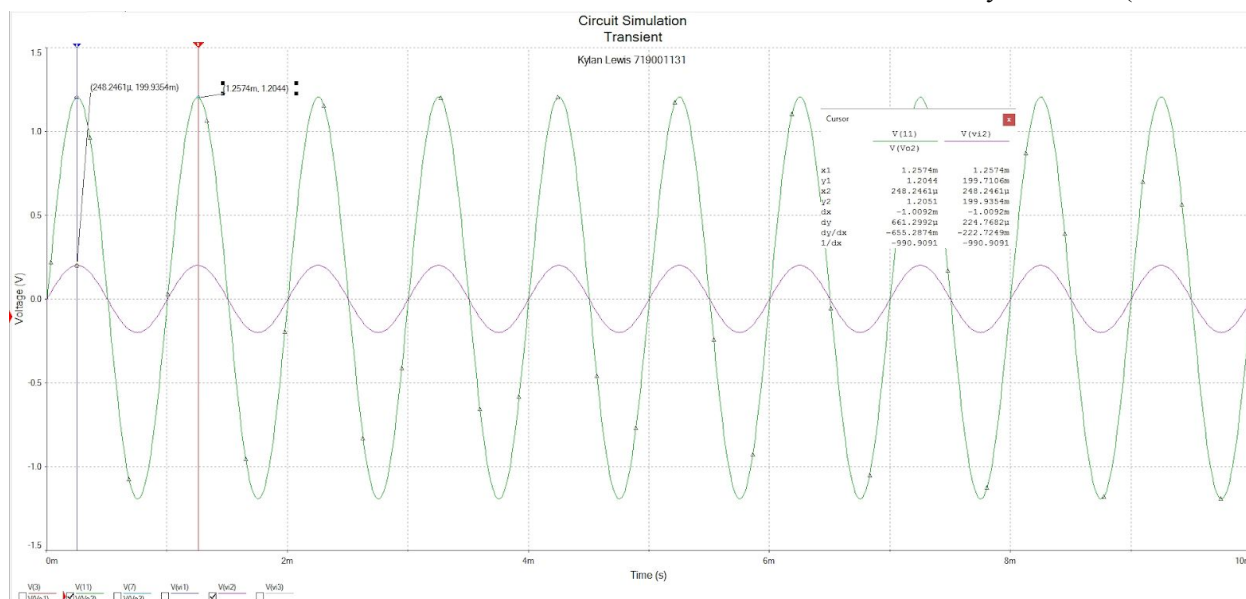


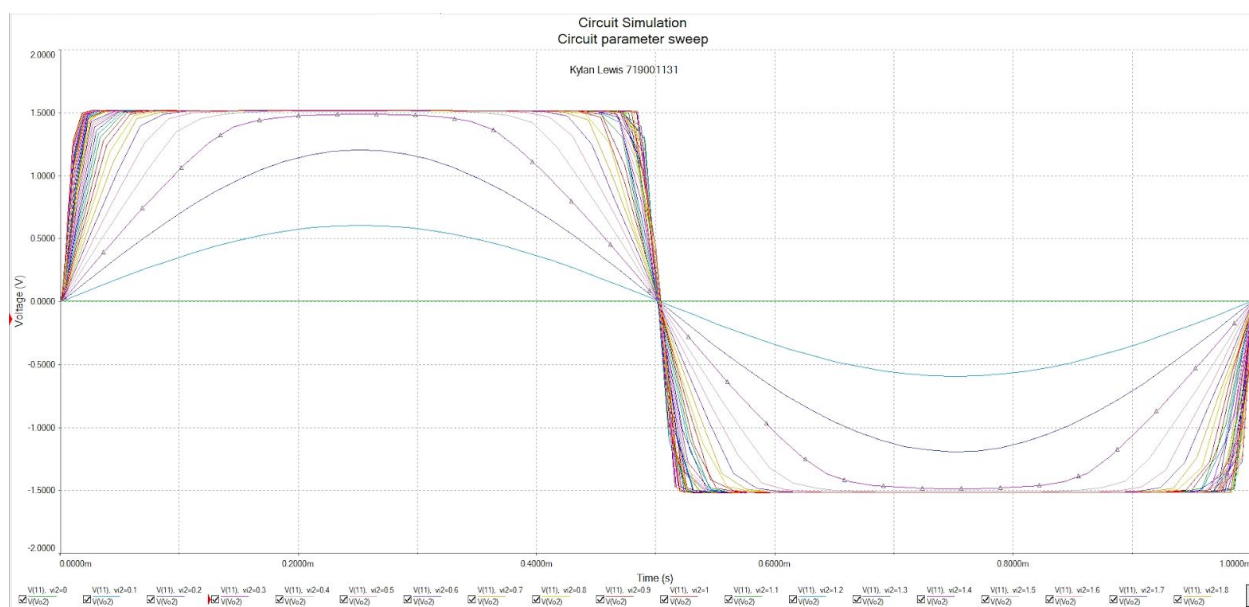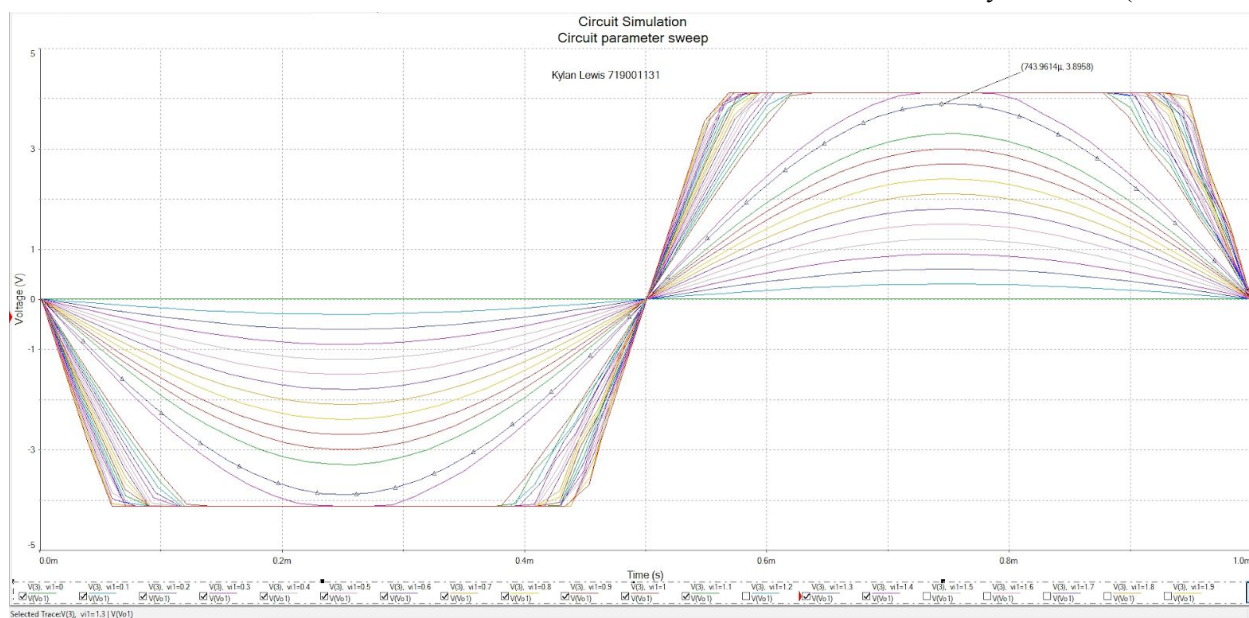3. Sweep from 0 to 5V at 1kHz using Transient





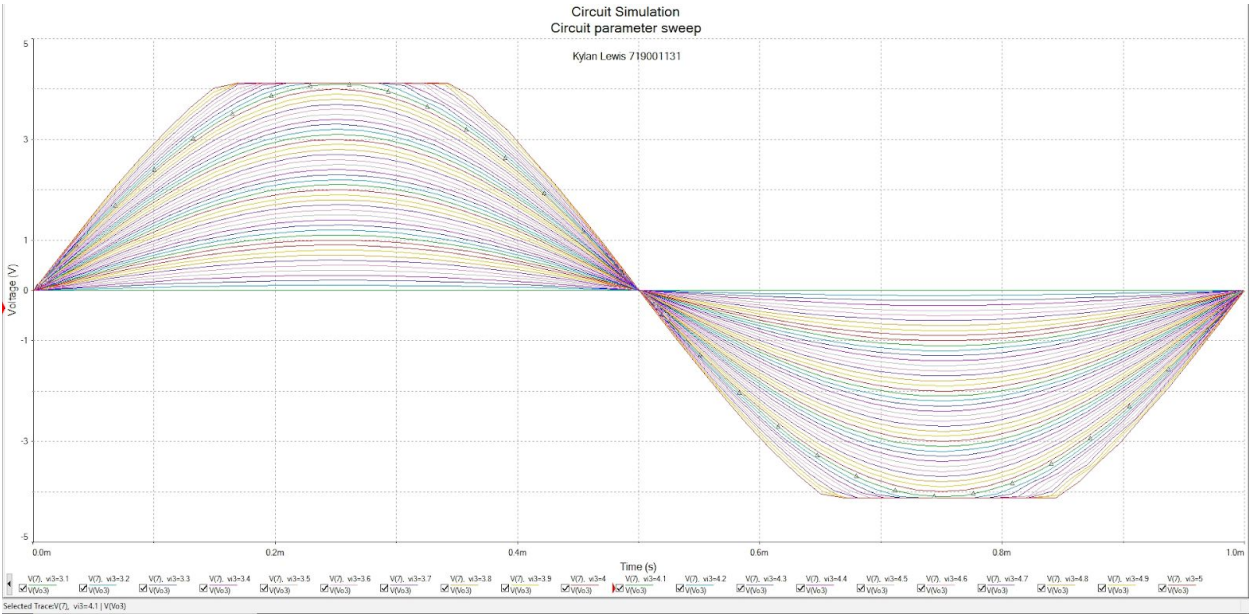

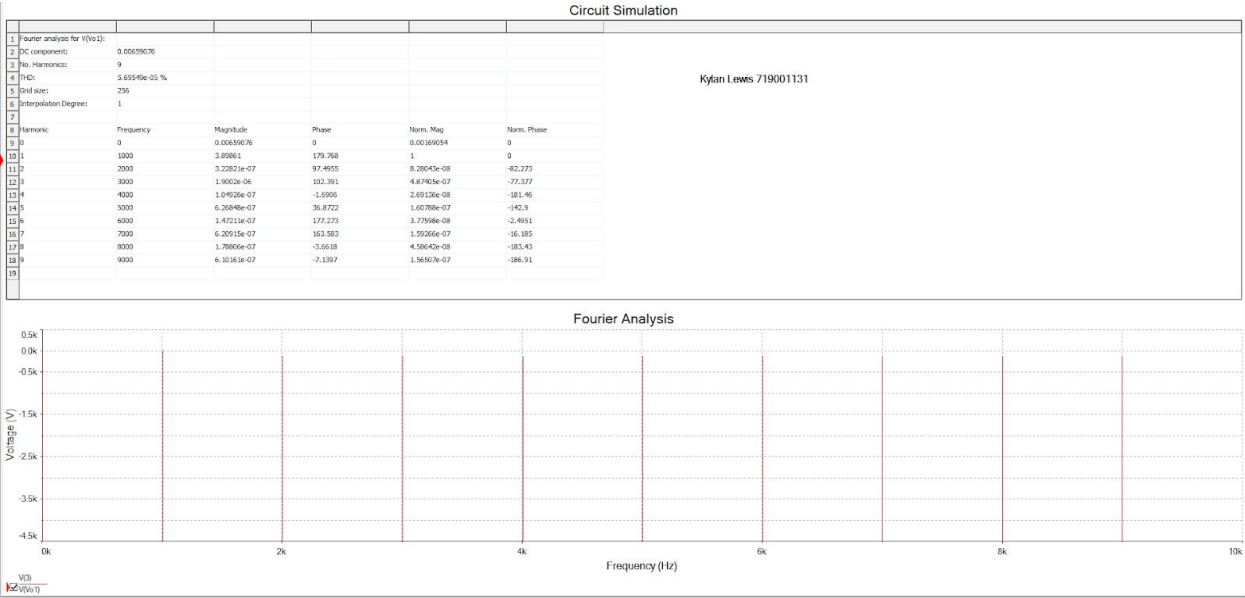4.  $V_i(t) = V_{i1} \max \sin(2\pi 1000t)$  using Fourier simulation





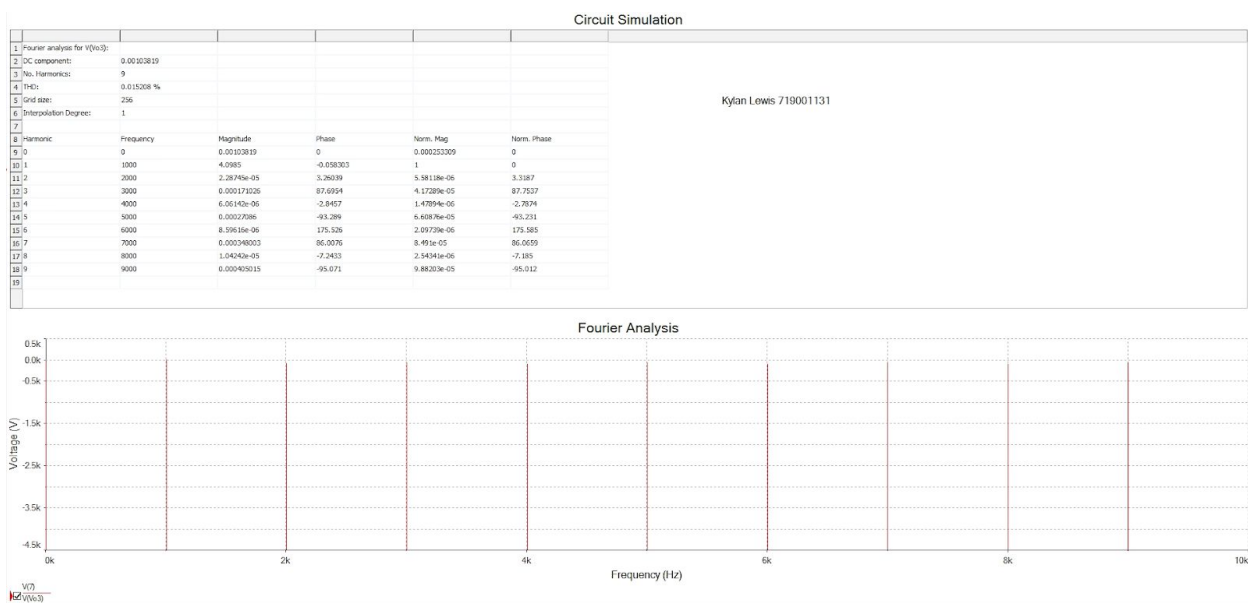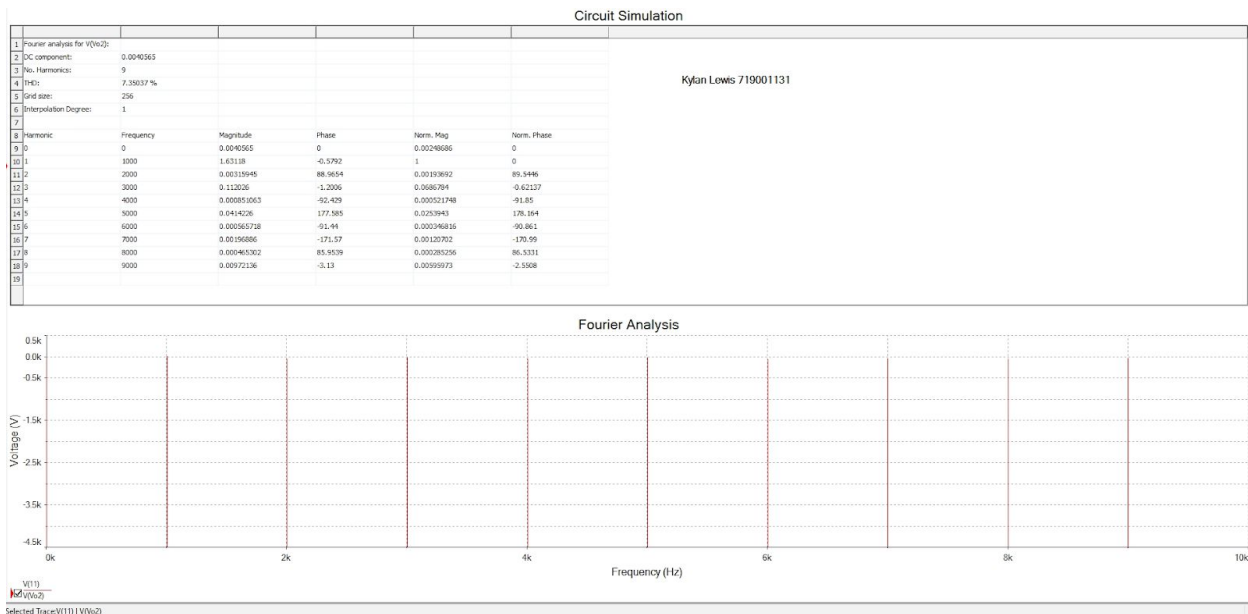

## TA Question:

Why did the student in the video use 200mV for amplitude when he plotted the Bode plot with a network analyzer?

The student chooses to use 200mV for the input amplitude when using the network analyzer because the maximum input amplitude is 0.5V. Anything over this would produce clipping and saturate the OpAmp. Also, he chooses the relatively small value 200mV which is the only option under 500mV and guarantees the amplifier Bode plot is linear.